

## Chapter 5

# Computer Architecture

These slides support chapter 5 of the book


*The Elements of Computing Systems*

(1<sup>st</sup> and 2<sup>nd</sup> editions)


By Noam Nisan and Shimon Schocken

MIT Press
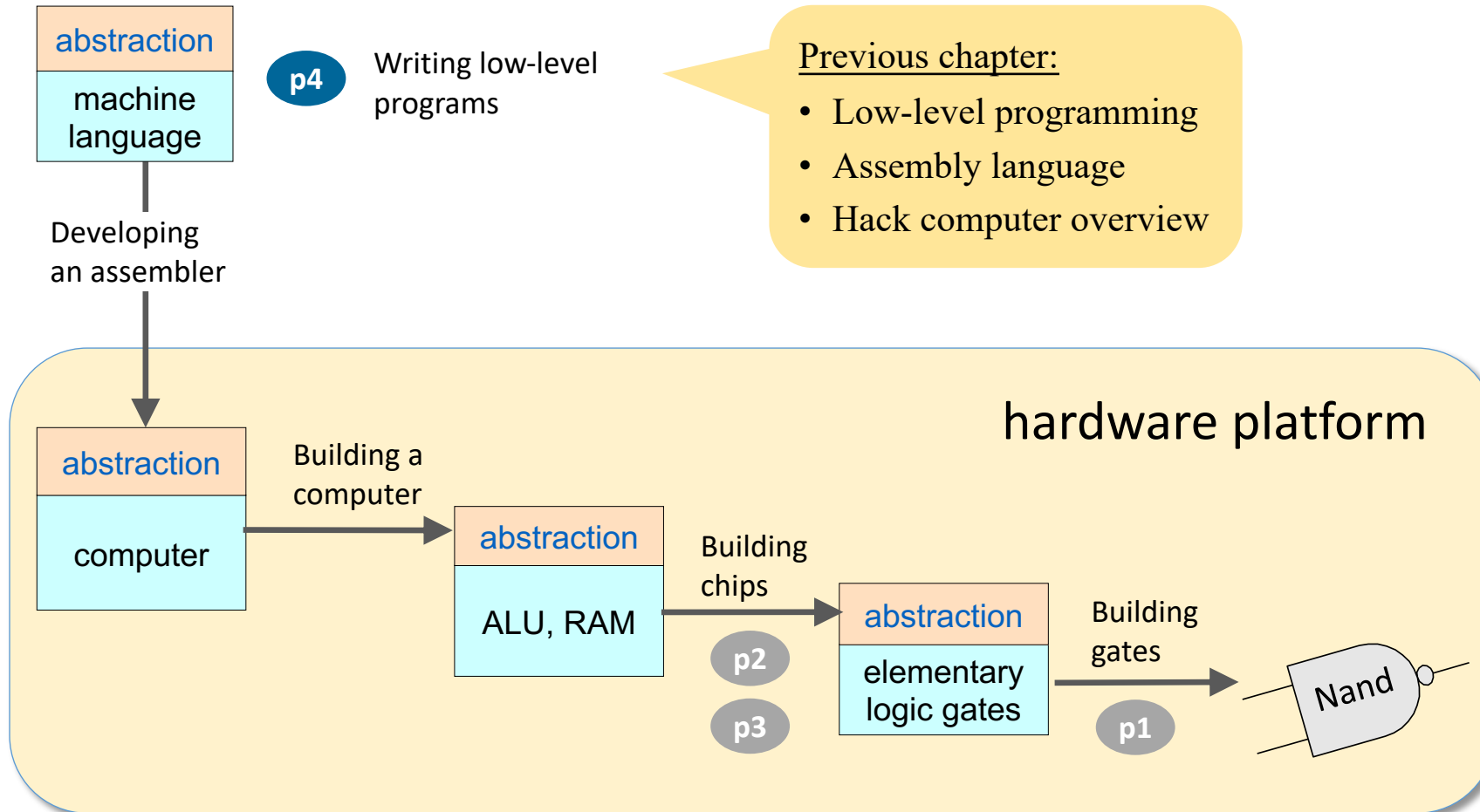
# Nand to Tetris Roadmap (Part I: Hardware)



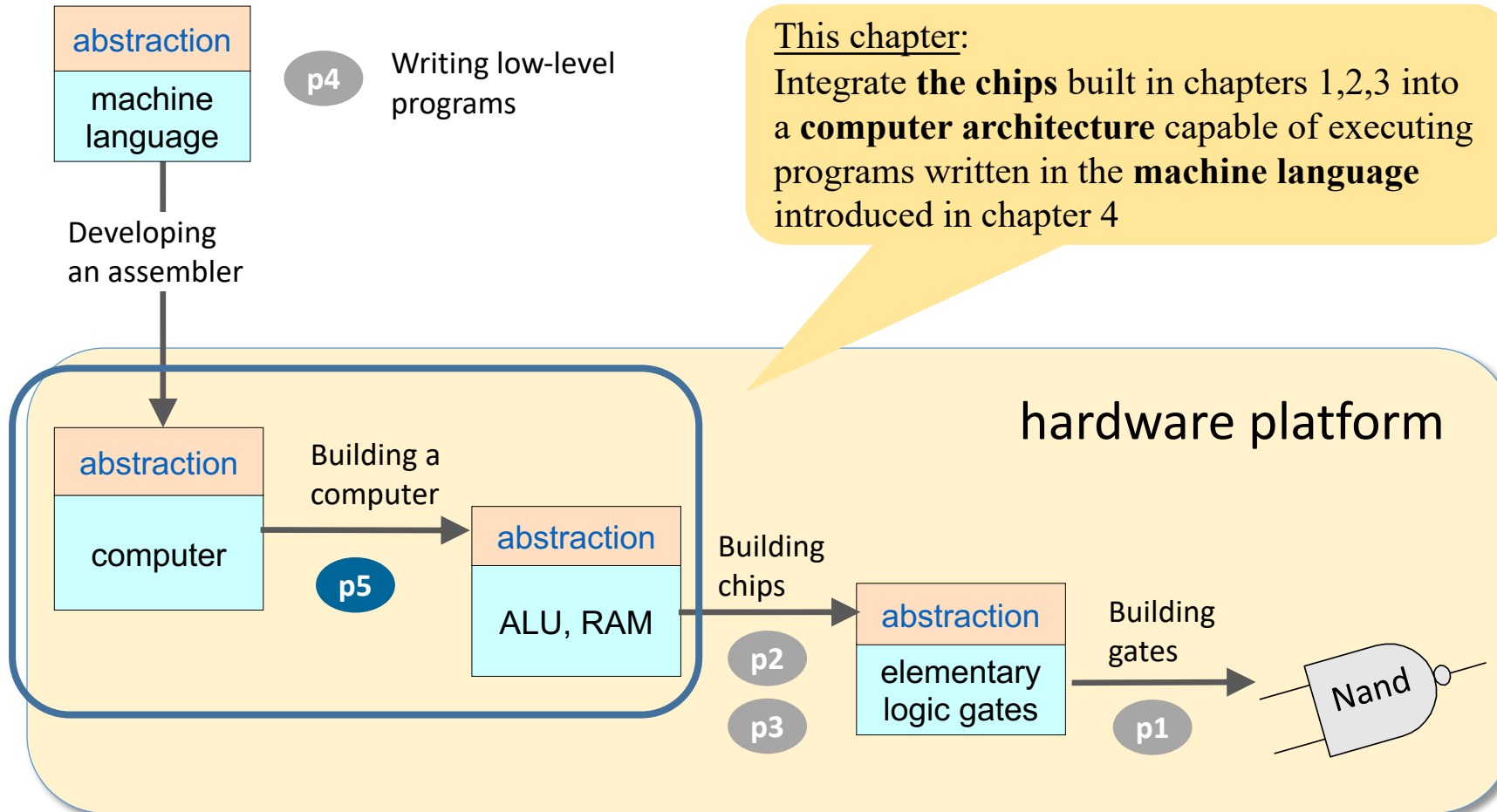
# Nand to Tetris Roadmap (Part I: Hardware)


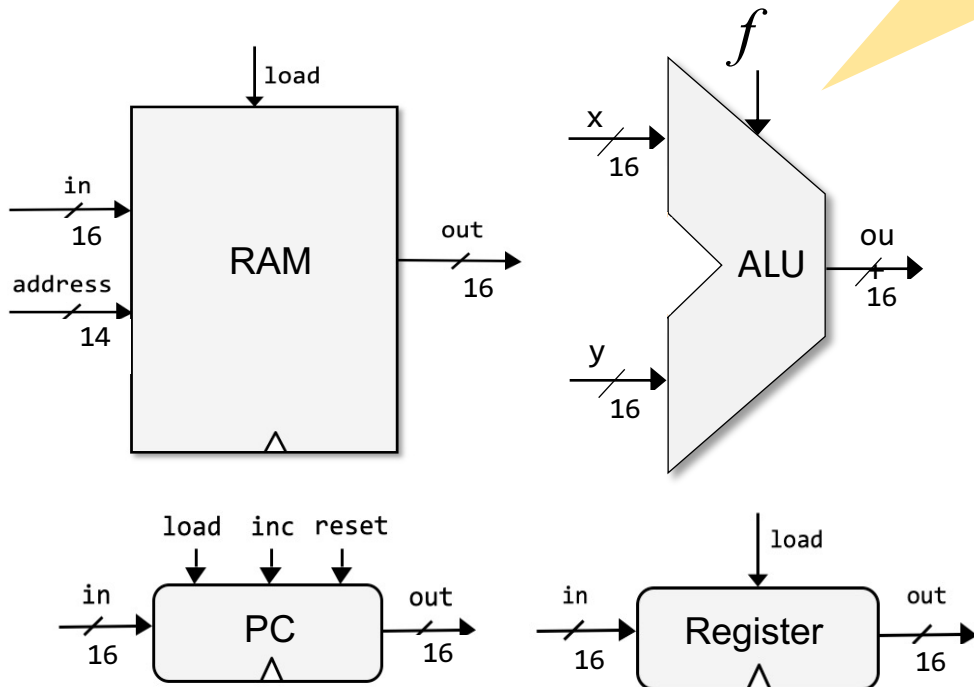
# Nand to Tetris Roadmap (Part I: Hardware)

This chapter:

Integrate **the chips** built in chapters 1,2,3 into a **computer architecture** capable of executing programs written in the **machine language** introduced in chapter 4




Machine language program (example)

```
// Computes R1 = 1 + 2 + 3 + ... + R0
// i = 1
@i
M=1
// sum = 0
@sum
M=0
(LOOP)
// if(i > R0) goto STOP
@i
D=M
@R0
D=D-M
@STOP
D;JGT
...
```

# Computer architecture

---

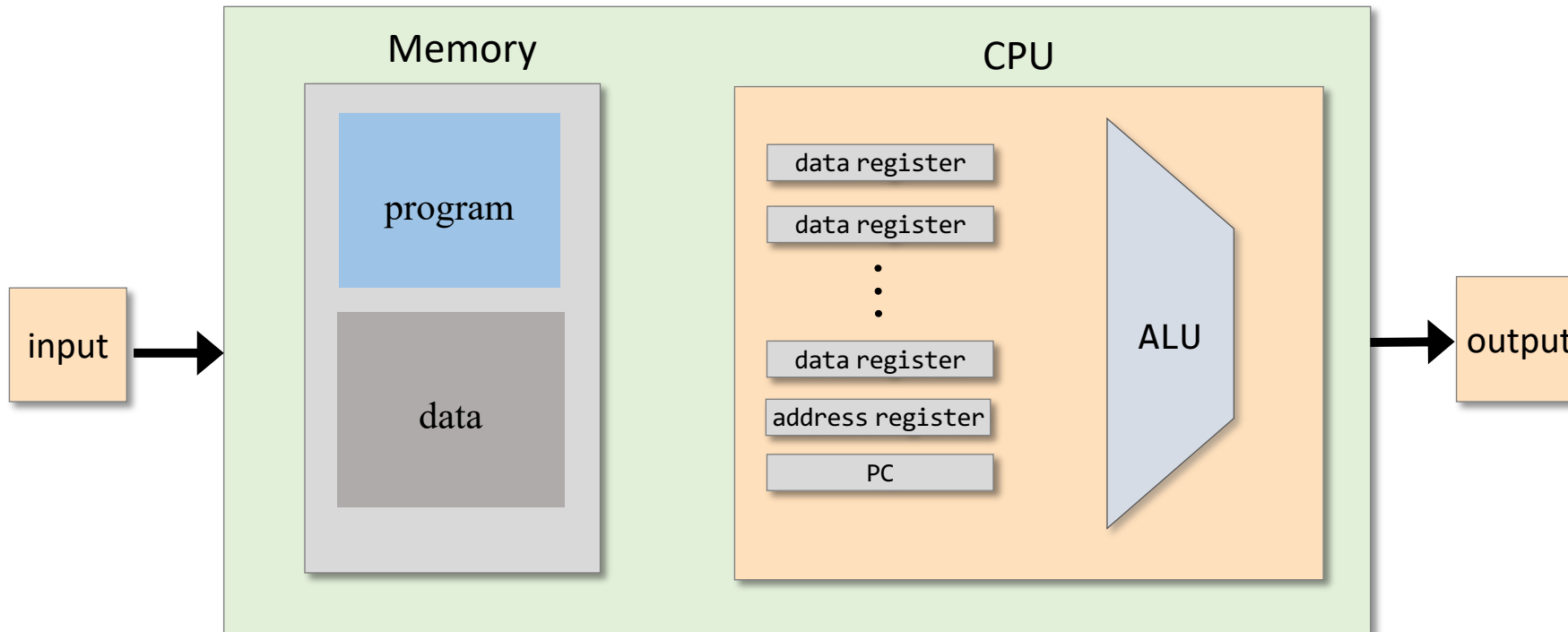

## Typical computer architecture:

- Stored program concept
- General-purpose

In this chapter we build the Hack computer – a variant of this architecture.

# Chapter 5: Computer Architecture

---

- Basic architecture
- Fetch-Execute cycle
- The Hack CPU
- Input / output
- Memory
- Computer
- Project 5: Chips
- Project 5: Guidelines

# Chapter 5: Computer Architecture

---



## Basic architecture

- Fetch-Execute cycle
- The Hack CPU
- Input / output
- Memory
- Computer
- Project 5: Chips
- Project 5: Guidelines

# Early computers (17<sup>th</sup> century)




Blaise Pascal  
1623-1662




## Pascal's Calculator (*Pascaline*, 1652)

- Add
- Subtract

 



 
# Early computers (17<sup>th</sup> century)




Gottfried Leibniz  
1646-1716

## Leibniz Calculator (1673)

- Add
- Subtract
- Multiply
- Divide.

 

 
# Early computers (17<sup>th</sup> century)



Gottfried Leibniz  
1646-1716

## Leibniz Calculator (1673)


- Add
- Subtract
- Multiply
- Divide.

 

Side benefits:  
Advances in  
gears /  
mechanical  
engineering


# Early computers (19<sup>th</sup> century)

---

 

Major innovation:  
Punched cards = software

Jacquard Loom (1804)

 


Analytic Engine (1837)



# Early computers

---

 

17<sup>th</sup> century: Hardware only / fixed / single purpose



Programmable!

19<sup>th</sup> century: Hardware / Software / General purpose

# Modern computers (20<sup>th</sup> century)

---



John Von Neumann



John Mauchly



Presper Eckert




John Atanassof



Howard Aiken




Konrad Zuse

 

ENIAC: First digital, programmable,  
stored program computer

 University of Pennsylvania, 1946,  
(Borrowed key ideas from other  
early computers and innovators)



Tommy Flowers


Colossus: First digital, programmable,  
computer, UK, 1945
 
# Modern computers (20<sup>th</sup> century)

---



Kathleen McNulty, Jean Jennings, Frances Snyder,  
Marlyn Wescoff, Frances Bilas, Ruth Lichterman



## ENIAC Women

Pioneered reusable code,  
subroutines, flowcharts,  
and many other programming  
innovations

Compilation  
pioneers  
(Mark I)



Grace Hopper



Adele Koss



# Modern computers (20<sup>th</sup> century)

---

Same **hardware** can run many different programs (**software**)




Back in the 1950's, this was considered a radical idea:

“If it should turn out that the basic logic of a machine designed for the numerical solution of differential equations coincides with the logic of a machine intended to make bills for department stores, I would regard this as the most amazing coincidence I have ever encountered” — Howard Aiken, 1956 (Mark 1 computer architect)

# Basic architecture

---

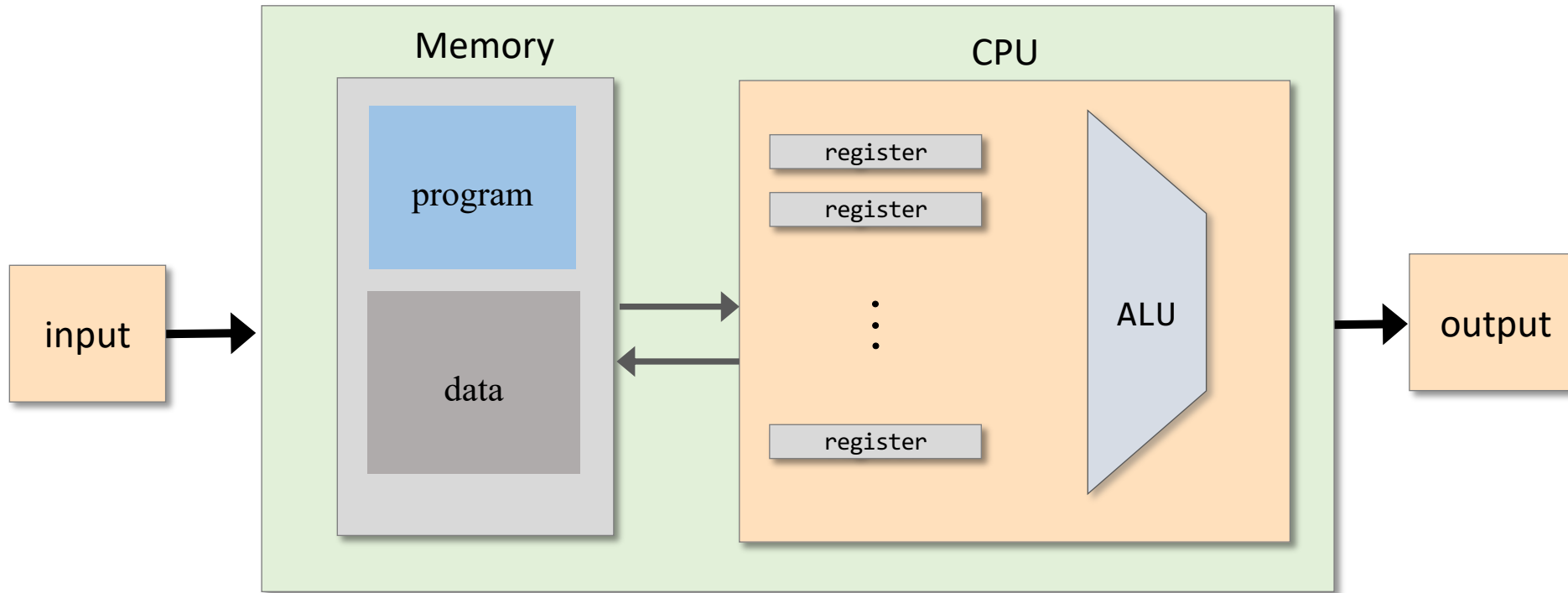

Stored program concept:


Same machine can run different programs

“The *stored program computer*, as conceived by Alan Turing and delivered by John von Neumann, broke the distinction between numbers that *mean things* and numbers that *do things*. Our universe would never be the same”. (George Dyson)



# Basic architecture


---

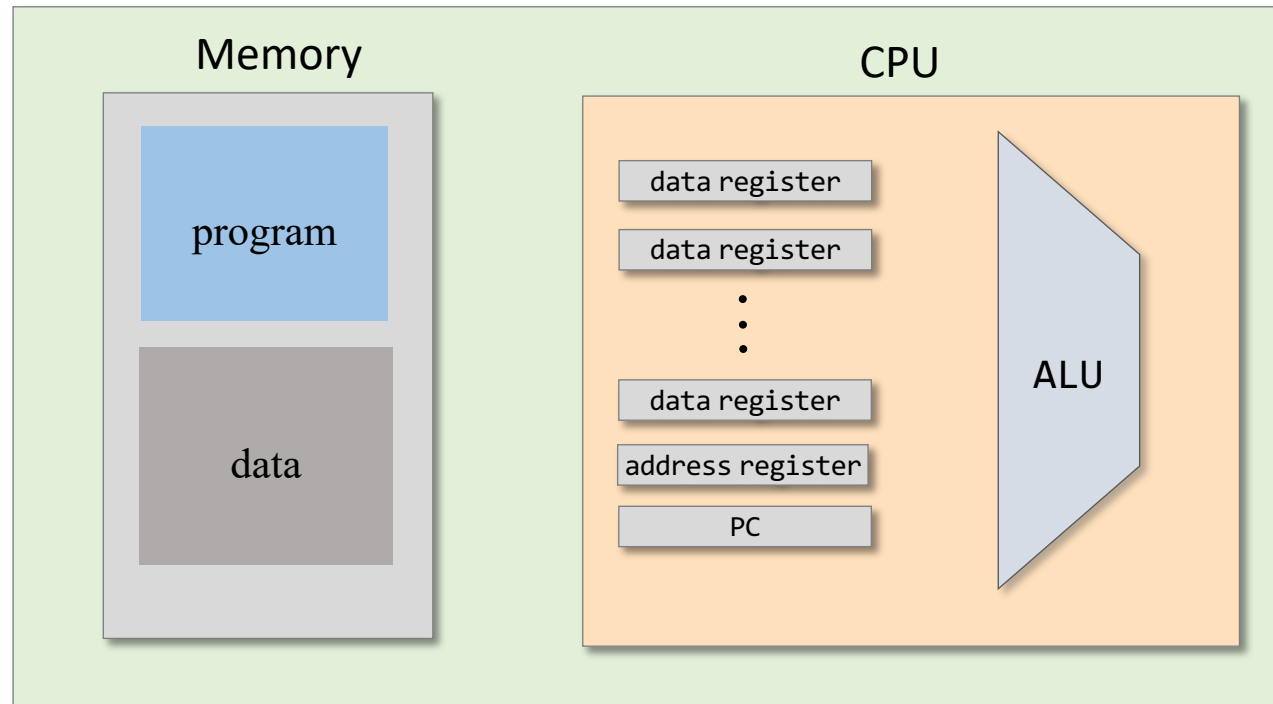

The computer is essentially a machine that manipulates *registers* under program control: *data* registers, *address* registers, a *program counter* (PC), *memory* registers (containing data and instructions).


How does information flow inside the computer?

# Basic architecture

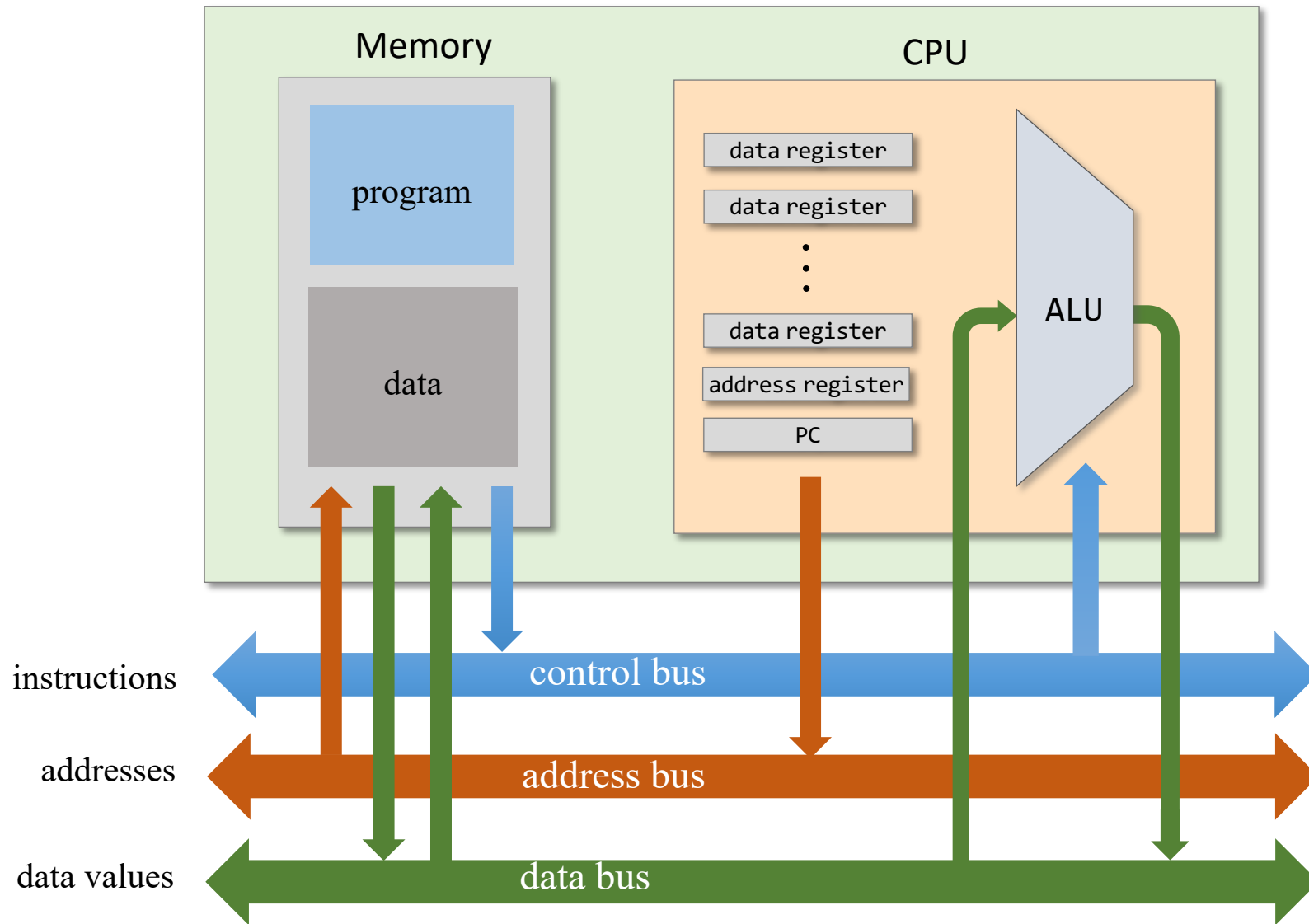

# Basic architecture: Recap

---

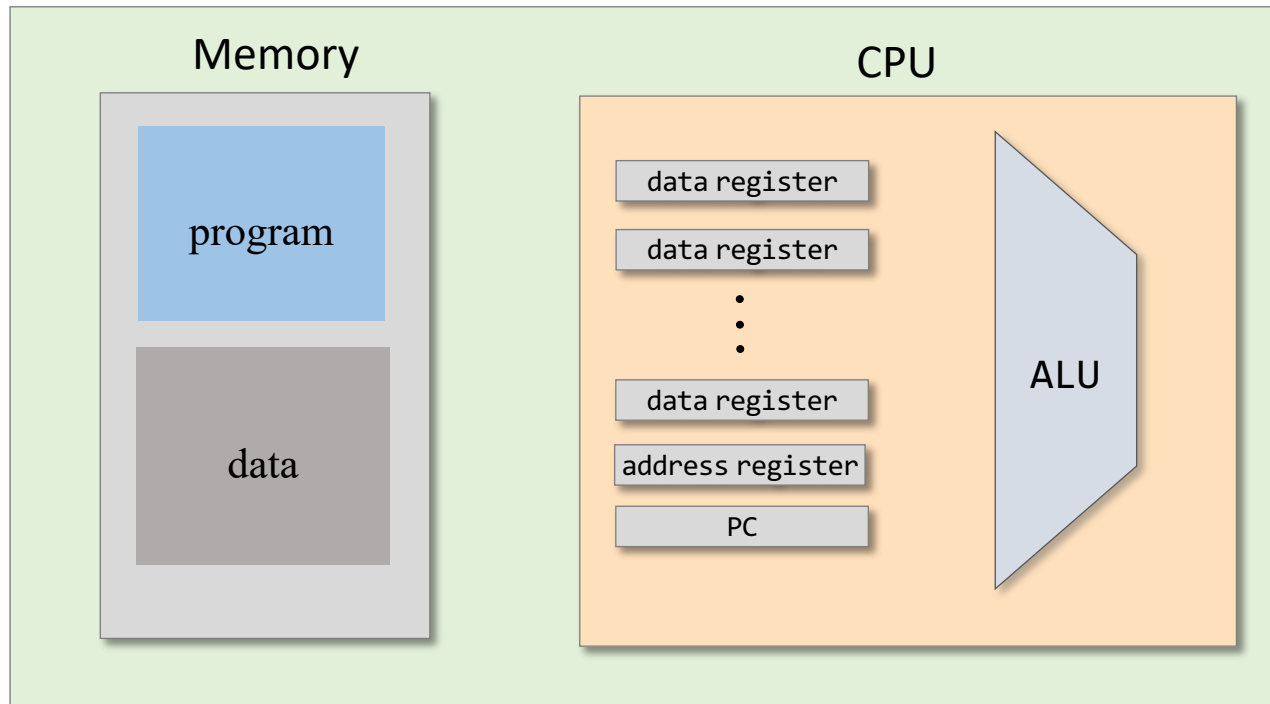

- General purpose computer
- A set of chips connected by buses
- Stored program concept
- Framework of most modern computers

# Chapter 5: Computer Architecture

---


✓ Basic architecture

➡ Fetch-Execute cycle


- The Hack CPU
- Input / output

- Memory
- Computer
- Project 5: Chips
- Project 5: Guidelines


# Computer architecture

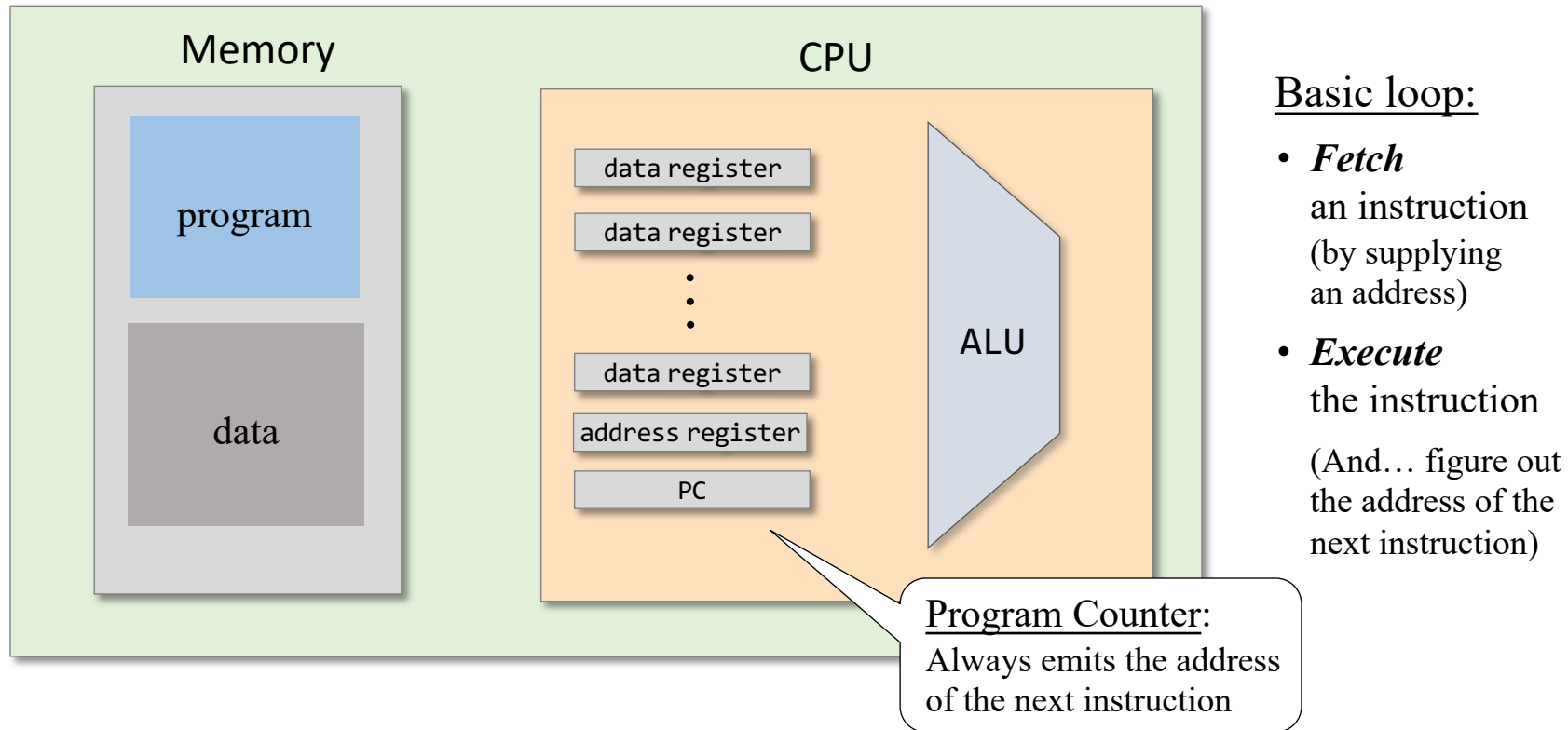


# Fetch an instruction

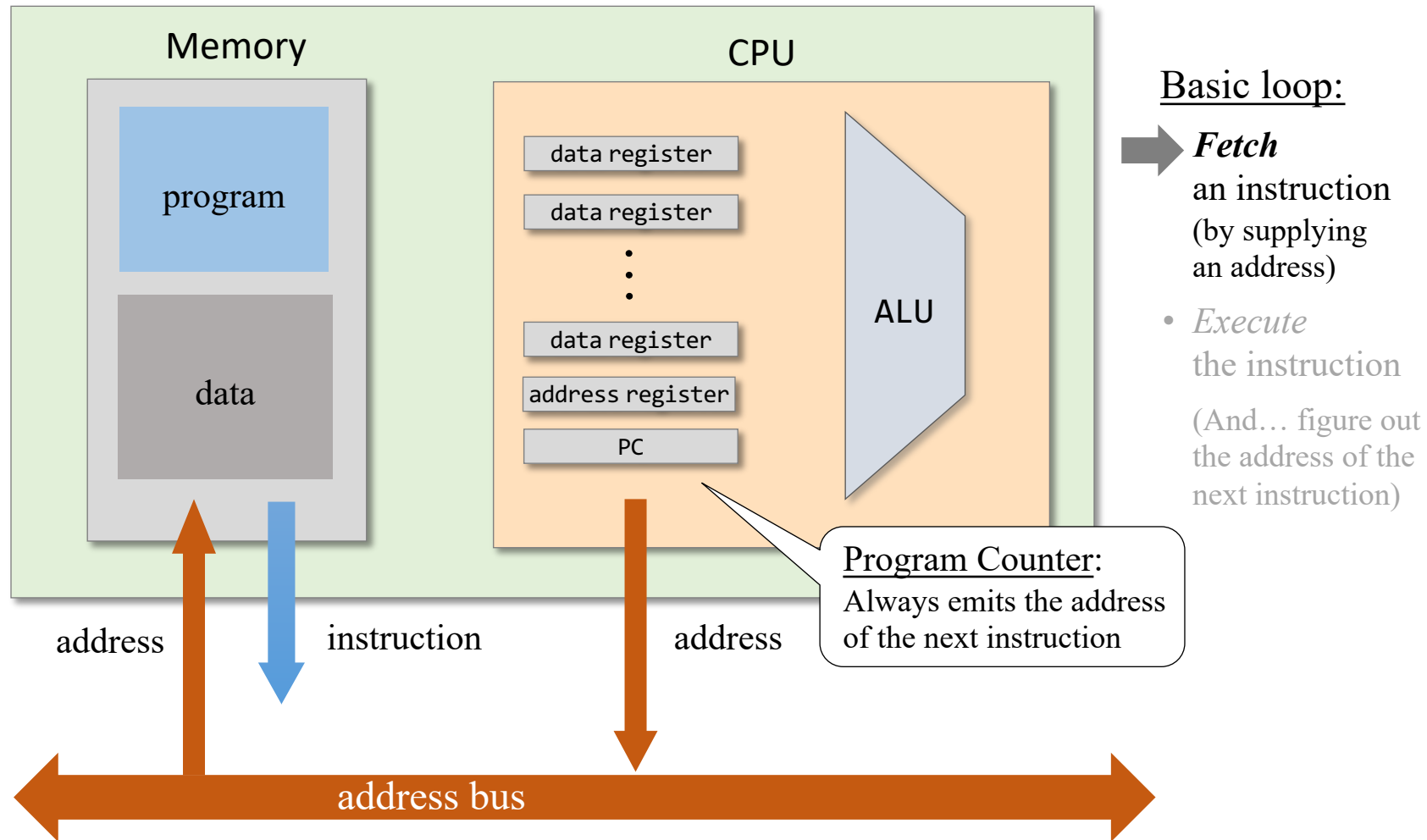

# Fetch an instruction

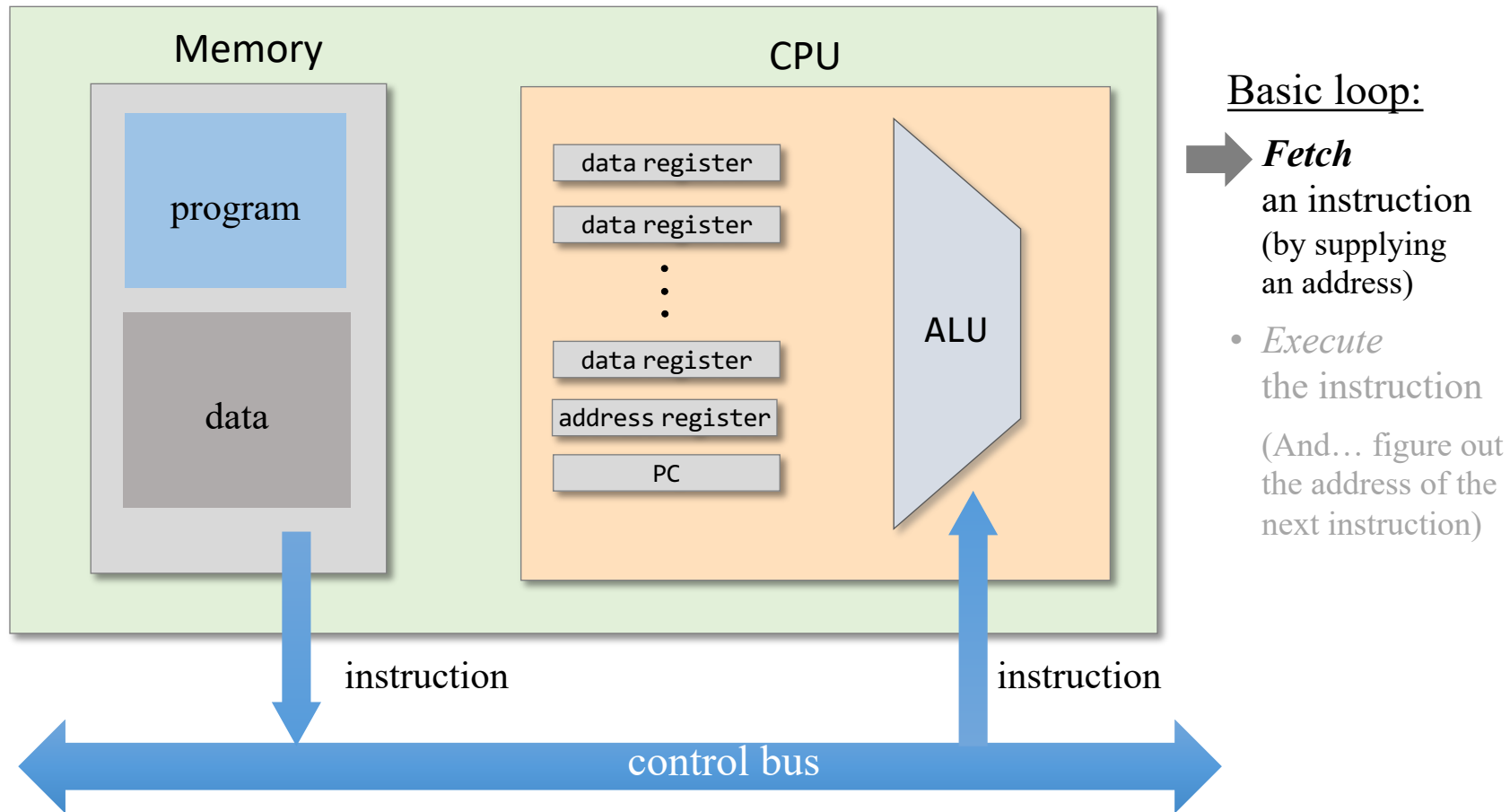


# Execute the instruction

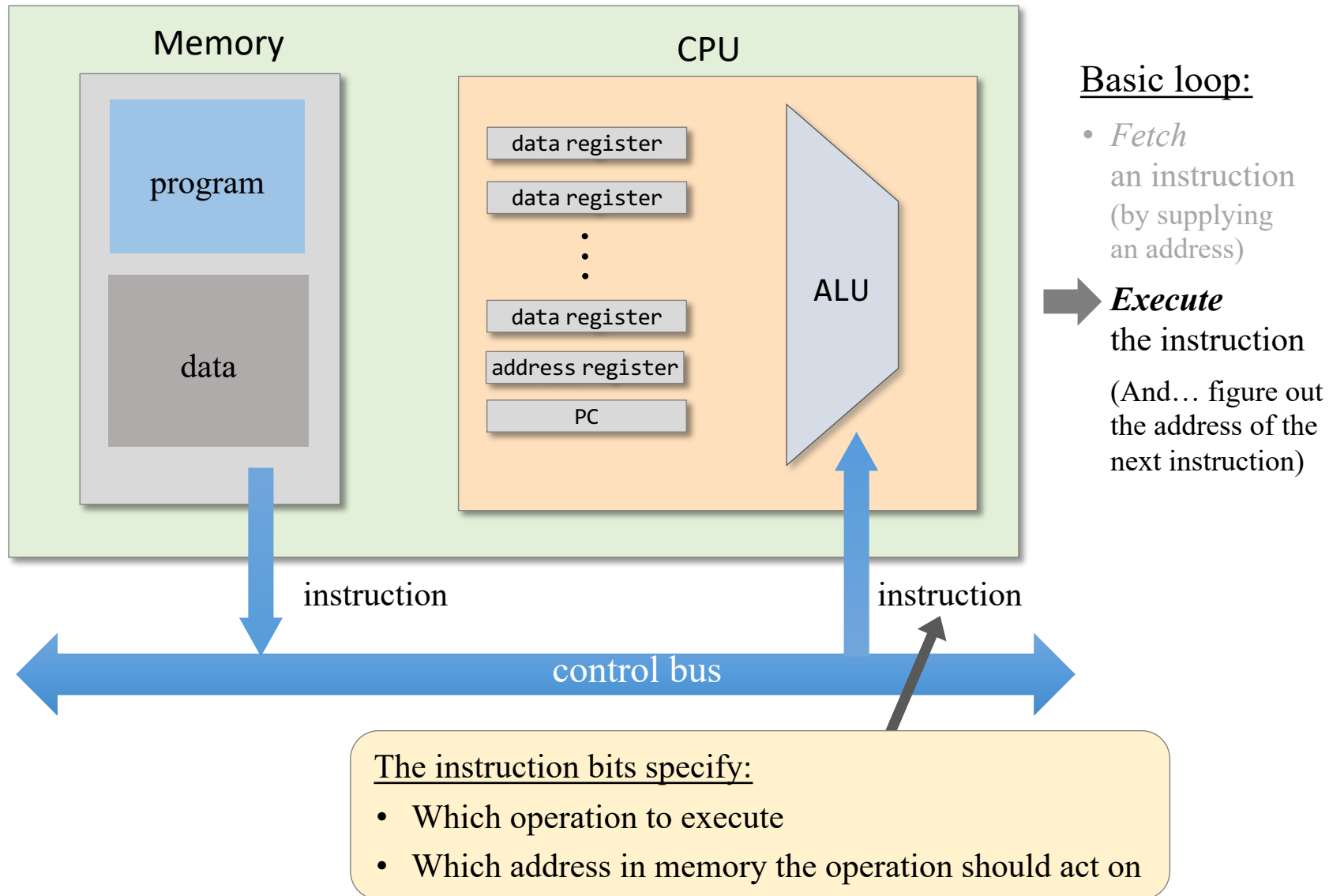




# Fetch – execute issues

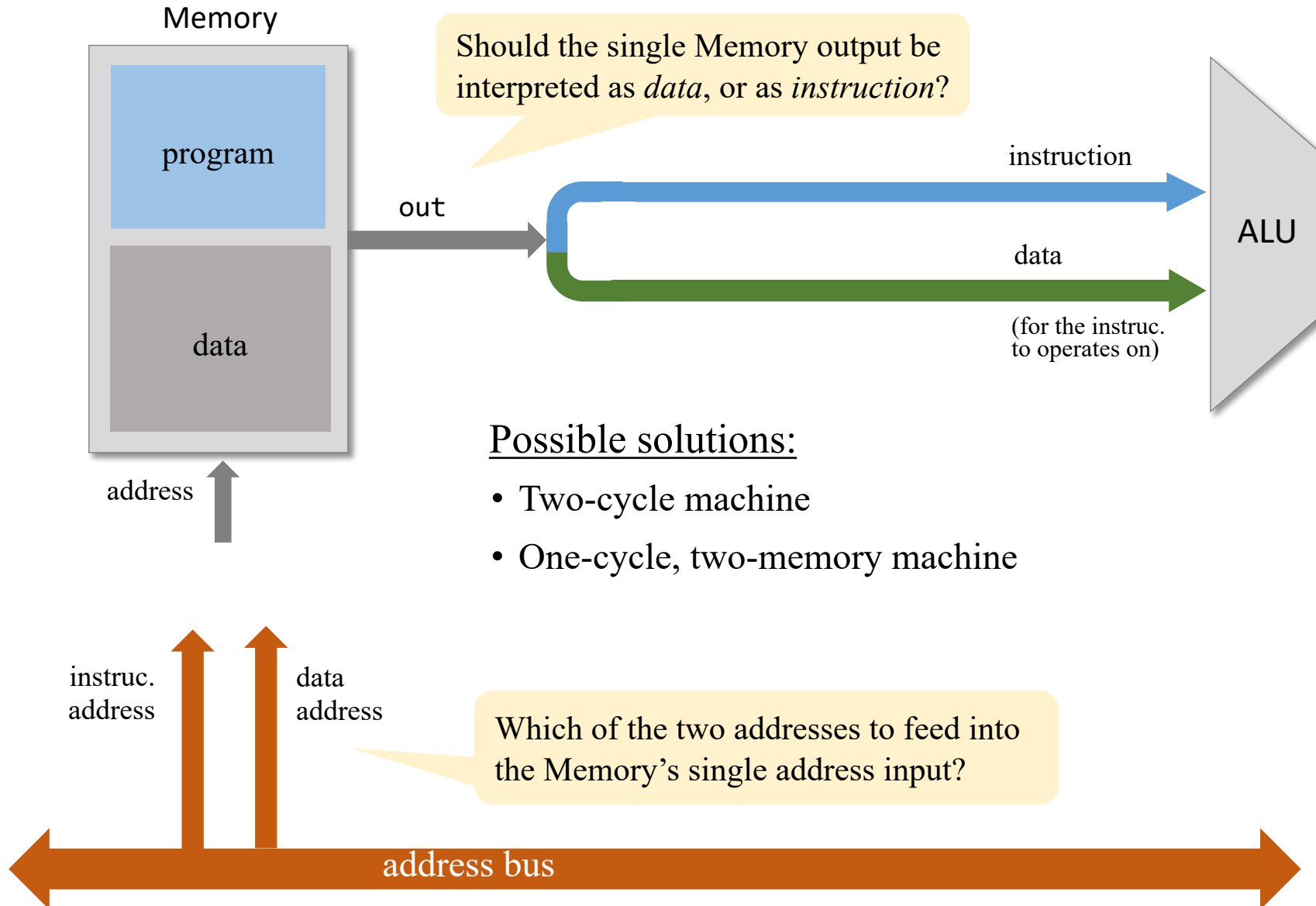


# Two-cycle machine

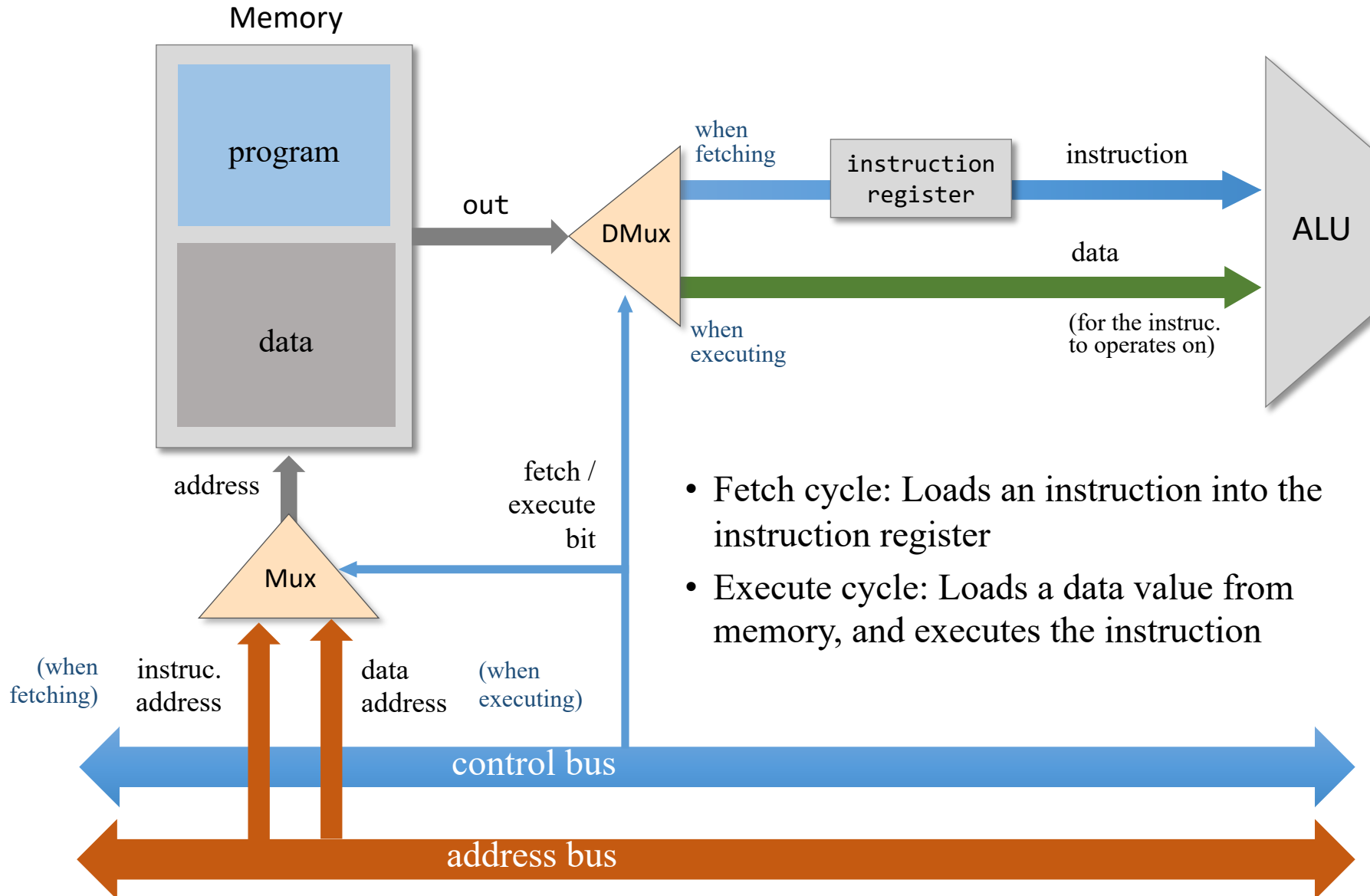

# Single cycle, two-memory machine


---

 

- Program and data are stored in two separate physical memories
- Both memories are accessed simultaneously, in the same cycle  
(Sometimes called "Harvard architecture")

# Single cycle, two-memory machine

---

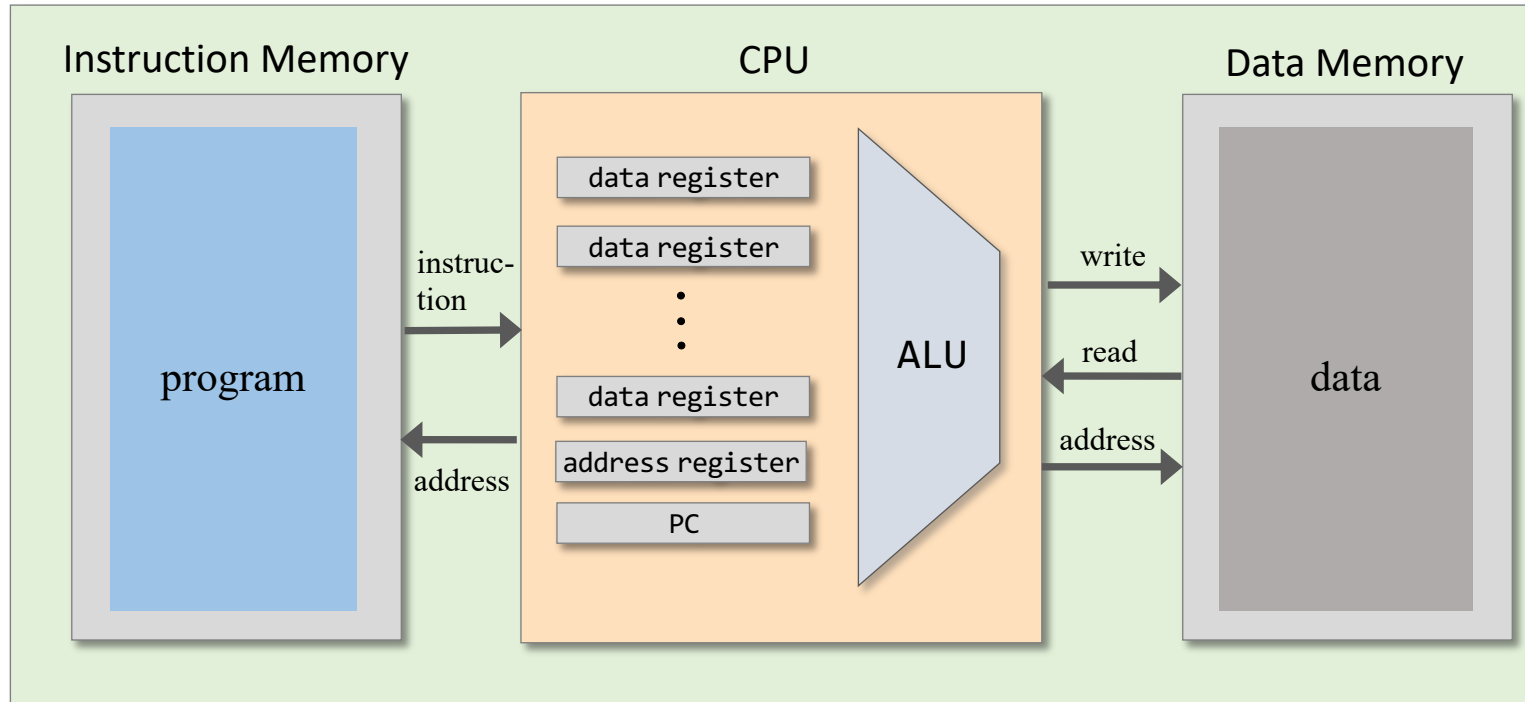

## Advantages

- Simpler architecture
- Faster processing

## Disadvantages

- Two memory chips
- Separate address spaces

# Chapter 5: Computer Architecture

---


- ✓ Basic architecture
- ✓ Fetch-Execute cycle

## The Hack CPU

- Input / output

- Memory
- Computer
- Project 5: Chips
- Project 5: Guidelines


# Hack computer

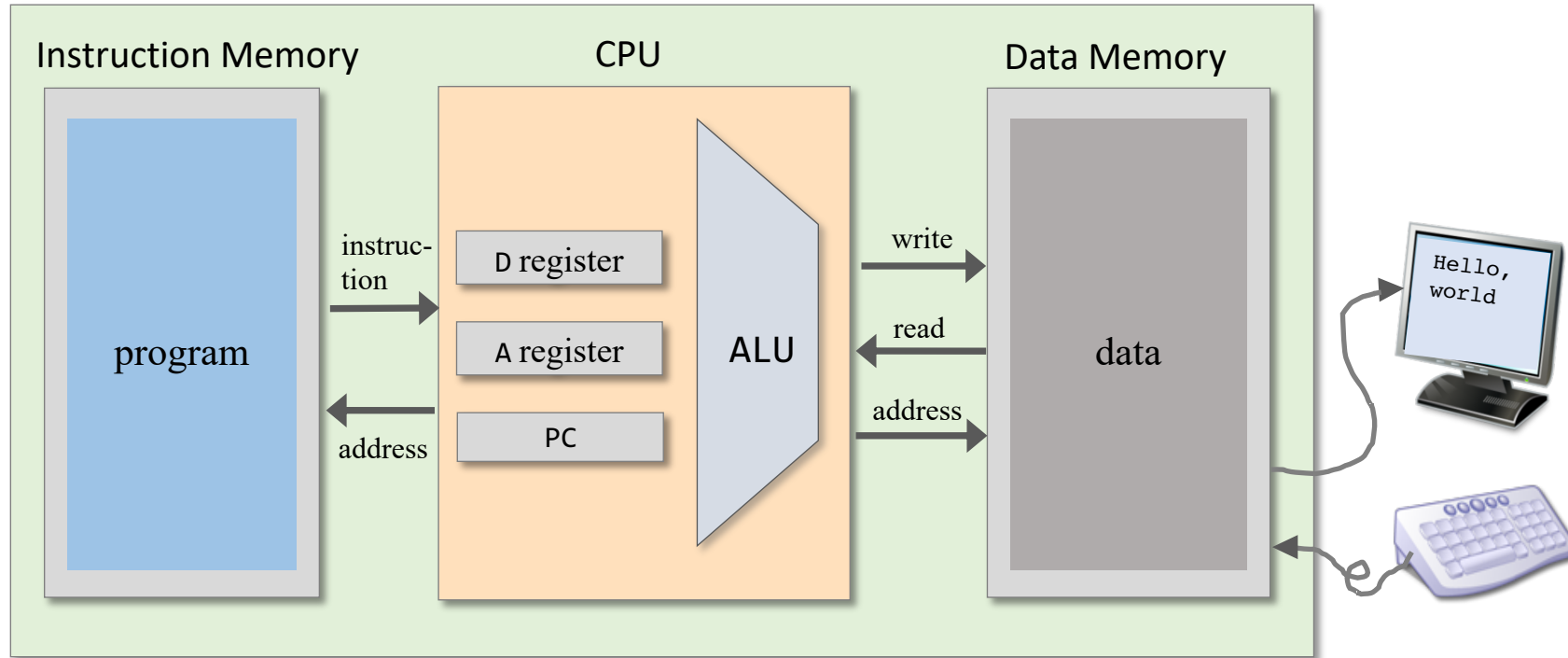


- Single cycle computer
- Two separate memory units

# Hack computer

---

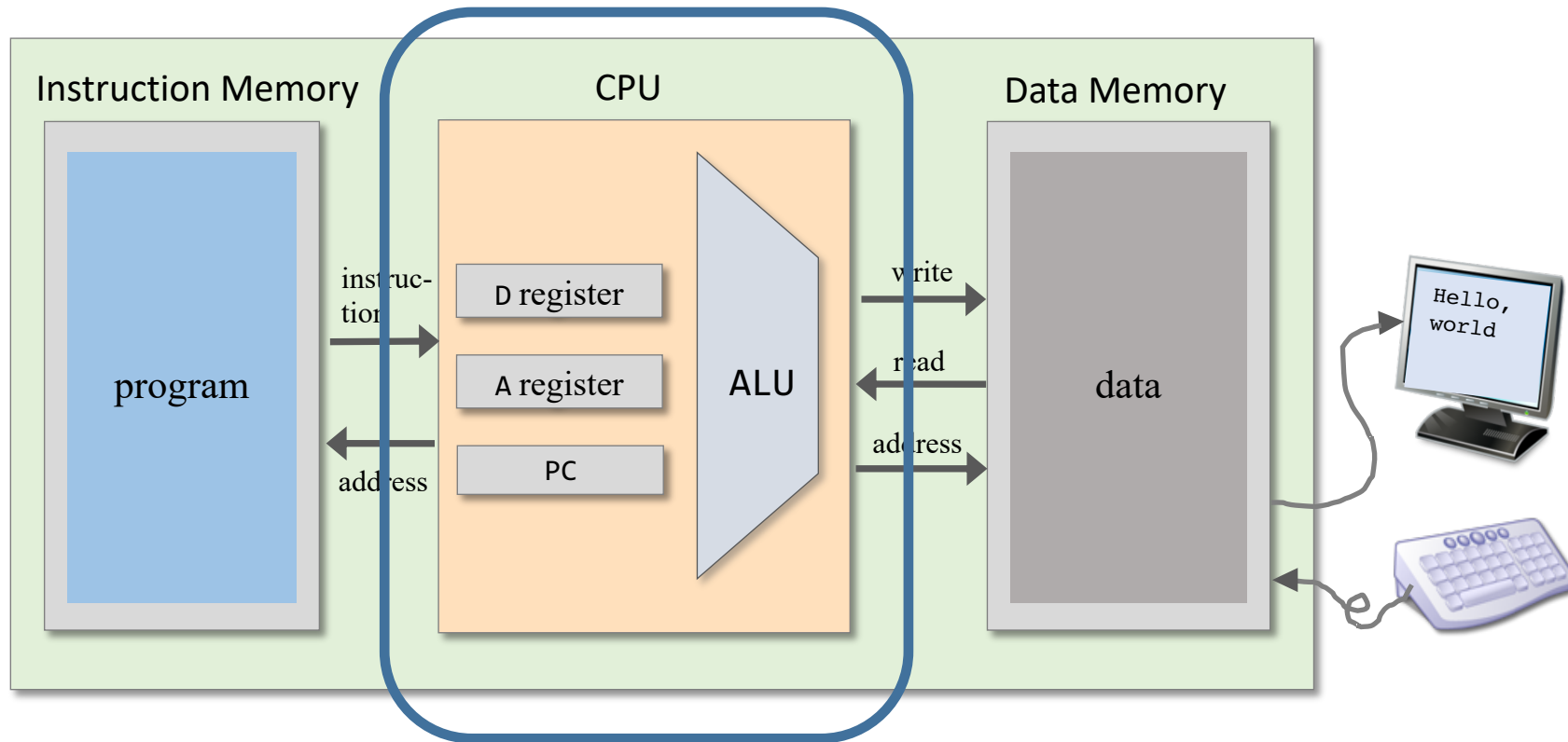

# CPU abstraction

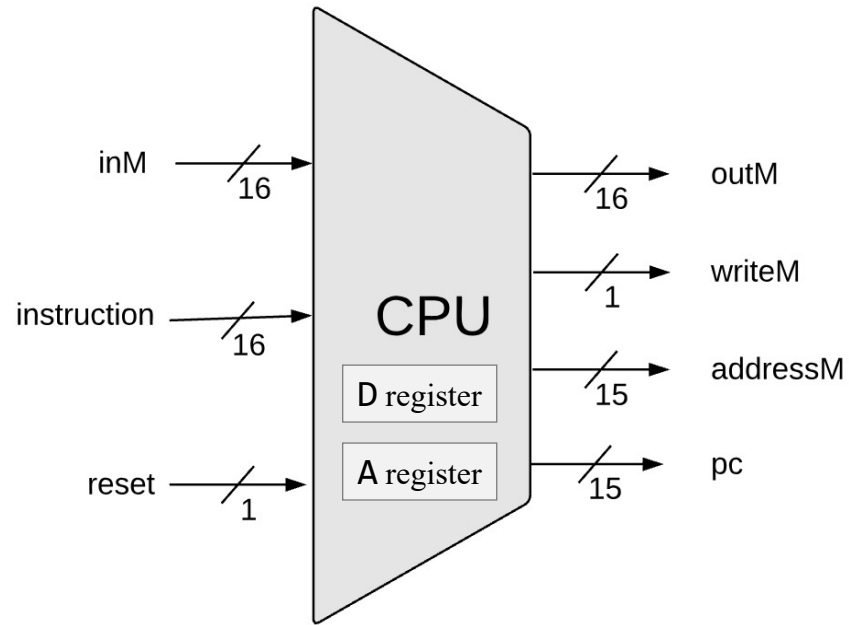

Instruction examples:

```
// D = RAM[5] + 1
@5
D=M+1
...
// RAM[3] = D
@3
M=D
...
```

## CPU Abstraction:

Executes instructions written in the Hack machine language



# CPU abstraction

## Hack instructions (formal specification)

### A instruction

Symbolic: @*xxx*

(*xxx* is a decimal value ranging from 0 to 32767,  
or a symbol bound to such a decimal value)

Binary: 0 *vvvvvvvvvvvvvvvv* (*vv ... v* = 15-bit value of *xxx*)

### C instruction

Symbolic: *dest = comp; jump*

(*comp* is mandatory.  
If *dest* is empty, the = is omitted;  
If *jump* is empty, the ; is omitted)


Binary: 111*ccccccddjjj*

<i>comp</i>		<i>c</i>	<i>c</i>	<i>c</i>	<i>c</i>	<i>c</i>	<i>c</i>	<i>dest</i>	<i>d</i>	<i>d</i>	<i>d</i>	Effect: store <i>comp</i> in:
0		1	0	1	0	1	0	null	0	0	0	the value is not stored
1		1	1	1	1	1	1	M	0	0	1	RAM[A]
-1		1	1	1	0	1	0	D	0	1	0	D register (reg)
D		0	0	1	1	0	0	DM	0	1	1	RAM[A] and D reg
A	M	1	1	0	0	0	0	A	1	0	0	A reg
!D		0	0	1	1	0	1	AM	1	0	1	A reg and RAM[A]
!A	!M	1	1	0	0	0	1	AD	1	1	0	A reg and D reg
-D		0	0	1	1	1	1	ADM	1	1	1	A reg, D reg, and RAM[A]
-A	-M	1	1	0	0	1	1					
D+1		0	1	1	1	1	1					
A+1	M+1	1	1	0	1	1	1					
D-1		0	0	1	1	1	0					
A-1	M-1	1	1	0	0	1	0					
D+A	D+M	0	0	0	0	1	0					
D-A	D-M	0	1	0	0	1	1					
A-D	M-D	0	0	0	1	1	1					
D&A	D&M	0	0	0	0	0	0					
D A	D M	0	1	0	1	0	1					

*a* == 0   *a* == 1

<i>jump</i>	<i>j</i>	<i>j</i>	<i>j</i>	Effect:
null	0	0	0	no jump
JGT	0	0	1	if <i>comp</i> > 0 jump
JEQ	0	1	0	if <i>comp</i> = 0 jump
JGE	0	1	1	if <i>comp</i> ≥ 0 jump
JLT	1	0	0	if <i>comp</i> < 0 jump
JNE	1	0	1	if <i>comp</i> ≠ 0 jump
JLE	1	1	0	if <i>comp</i> ≤ 0 jump
JMP	1	1	1	unconditional jump

# CPU abstraction

 

Instruction examples:


```
// D = RAM[5] + 1
@5
D=M+1
...
// RAM[3] = D
@3
M=D
...
```

## CPU Abstraction:

Executes instructions written in the Hack machine language

Note that the selected memory register  $M$  can be input, or output, or both input and output (example:  $M=M+1$ )

# CPU abstraction

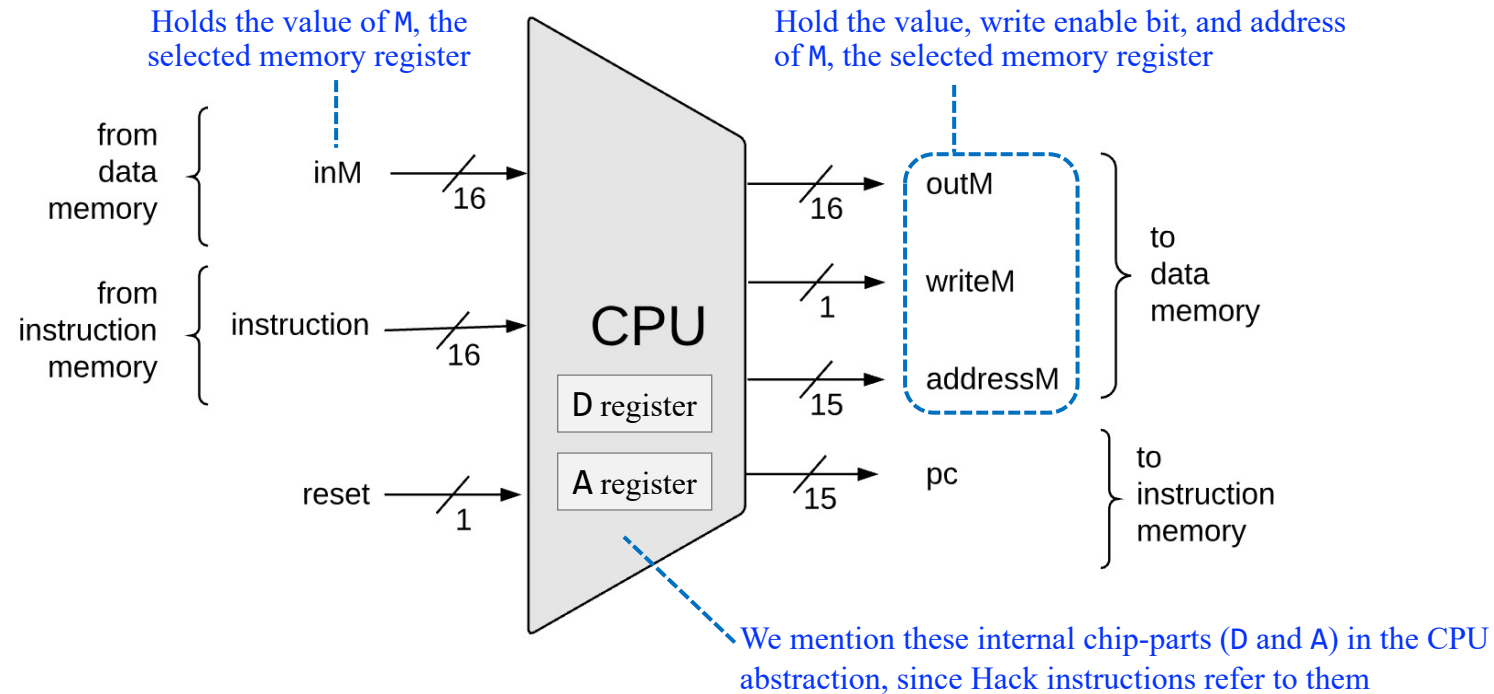

Instruction examples:


```
// D = RAM[5] + 1
@5
D=M+1
...
// RAM[3] = D
@3
M=D
...
```

## CPU Abstraction:

Executes instructions written in the Hack machine language

Note that the selected memory register M can be input, or output, or both input and output (example:  $M=M+1$ )

# CPU abstraction

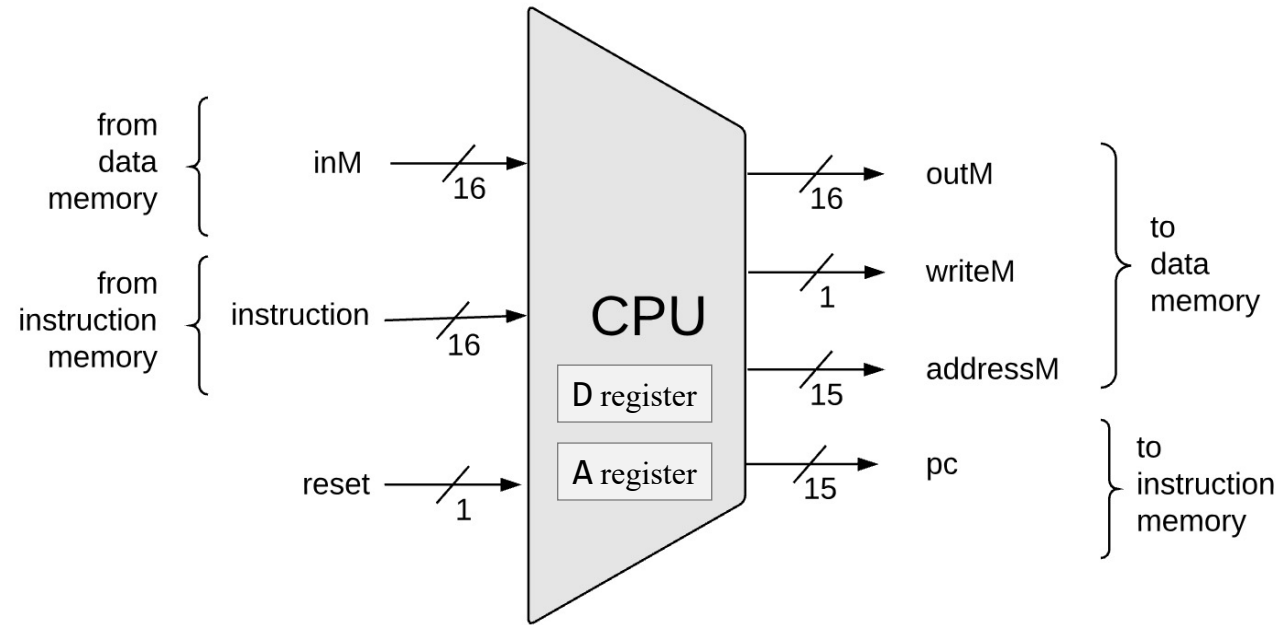

## CPU operation:

Instruction examples:

```
// D = RAM[5] + 1
@5
D=M+1
...
// RAM[3] = D
@3
M=D
...
```

### 1. Executes the instruction:


If it's an A instruction (@xxx), sets the A register to xxx

Else:


- If the instruction uses M as input, gets this value from inM
- Computes the ALU function specified by the instruction
- If the instruction writes to M, puts the ALU output in outM, puts the register's address in addressM, and asserts the writeM bit

### 2. Figures out the address of the next instruction, and puts it in pc.


# CPU implementation

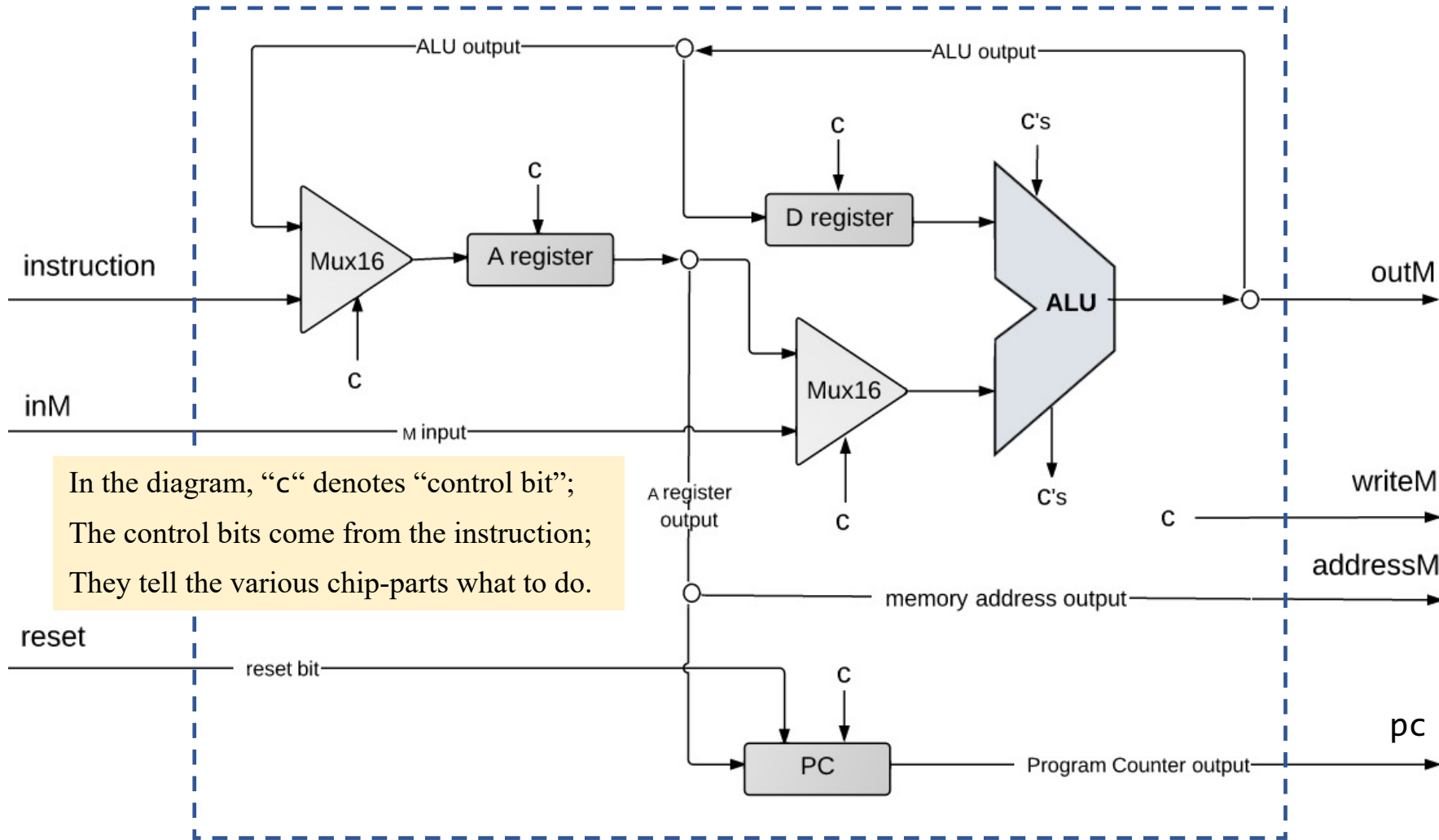

# CPU implementation

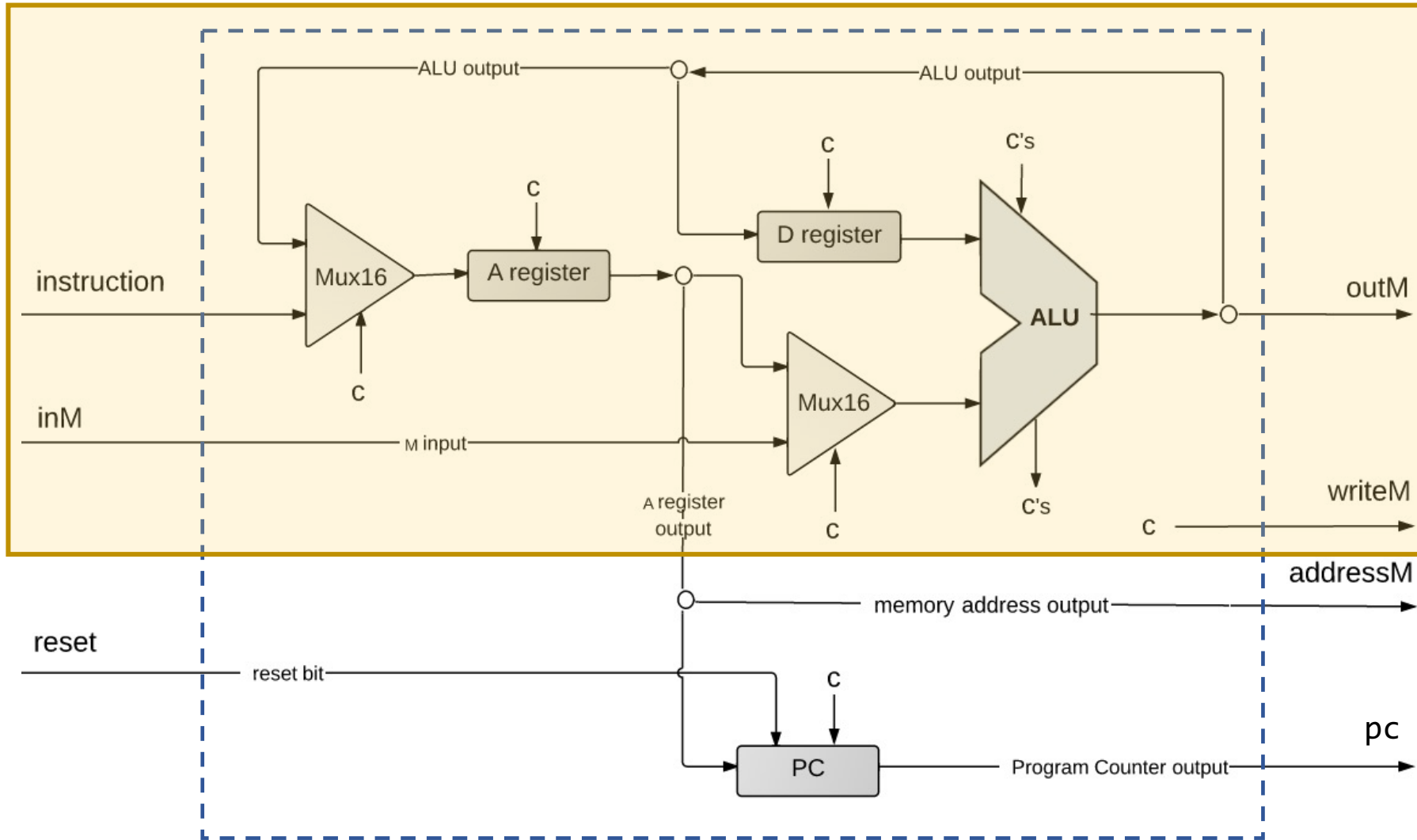

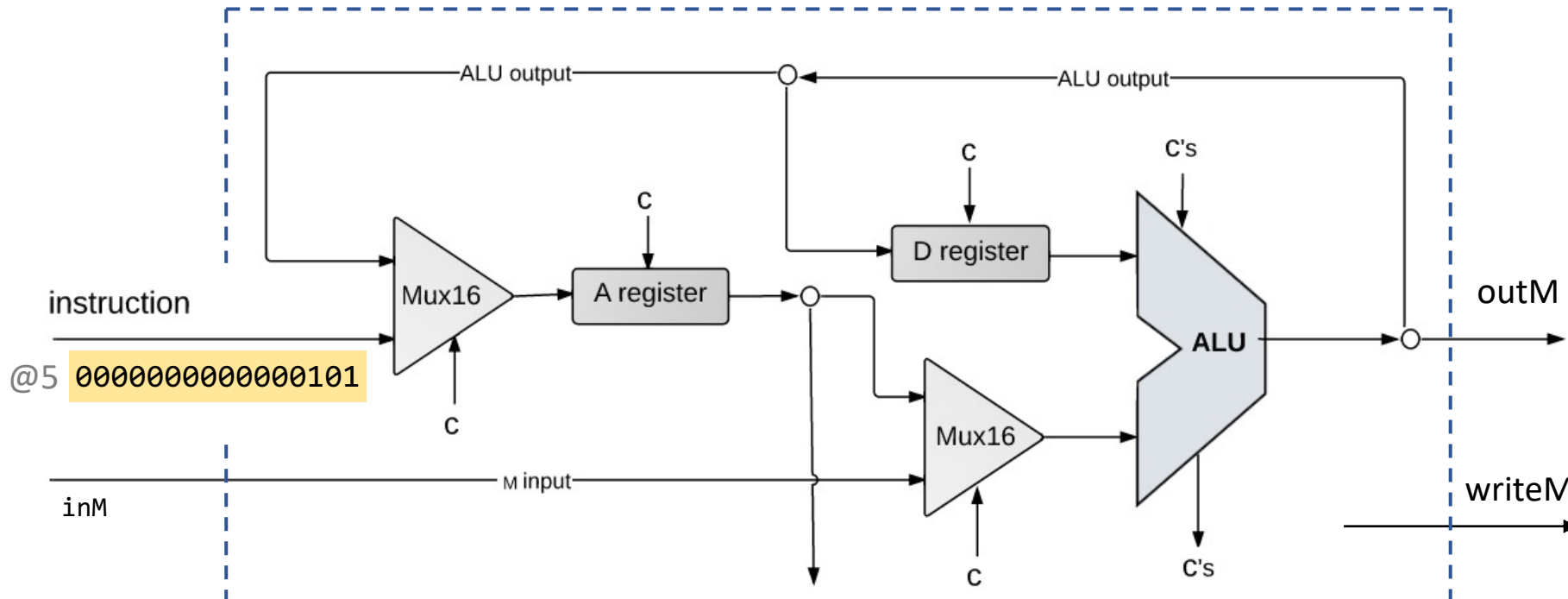
# CPU implementation: Instruction handling



## Handling A-instructions

Routes the instruction's MSB (op-code) to the Mux16 control bit
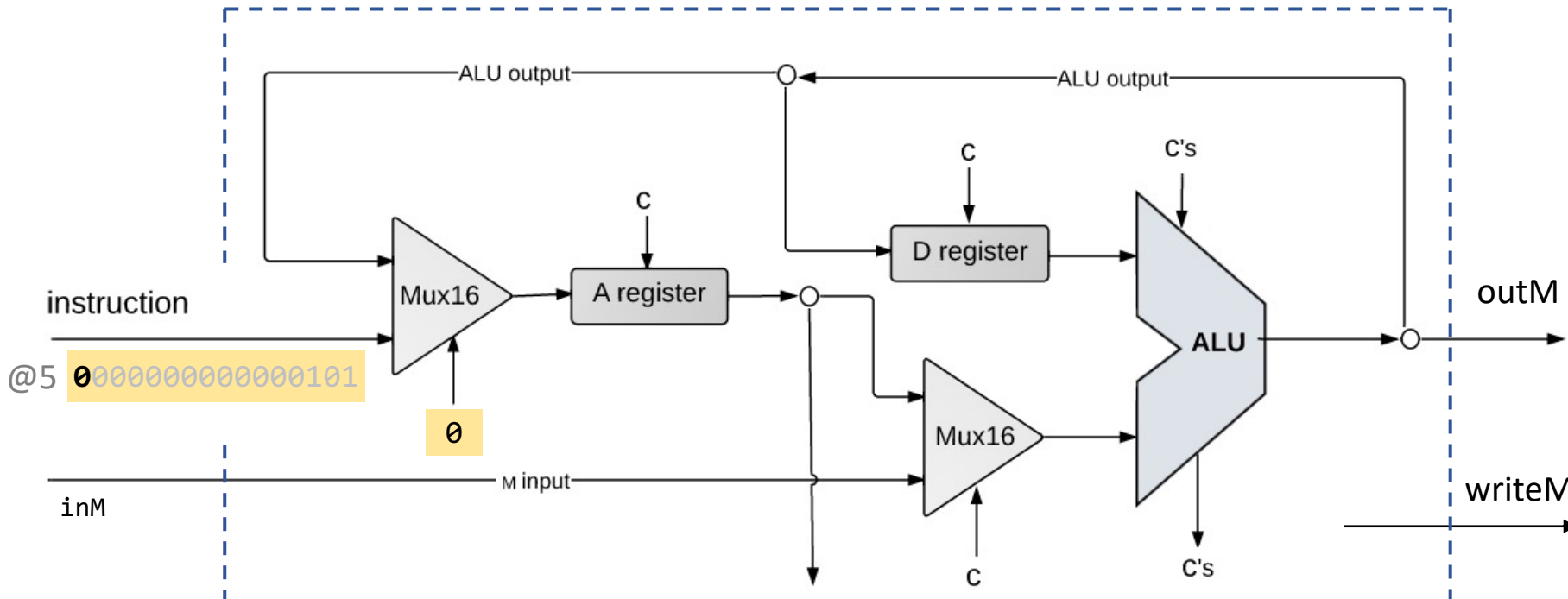
# CPU implementation: Instruction handling




## Handling A-instructions

Routes the instruction's MSB (op-code) to the Mux16 control bit


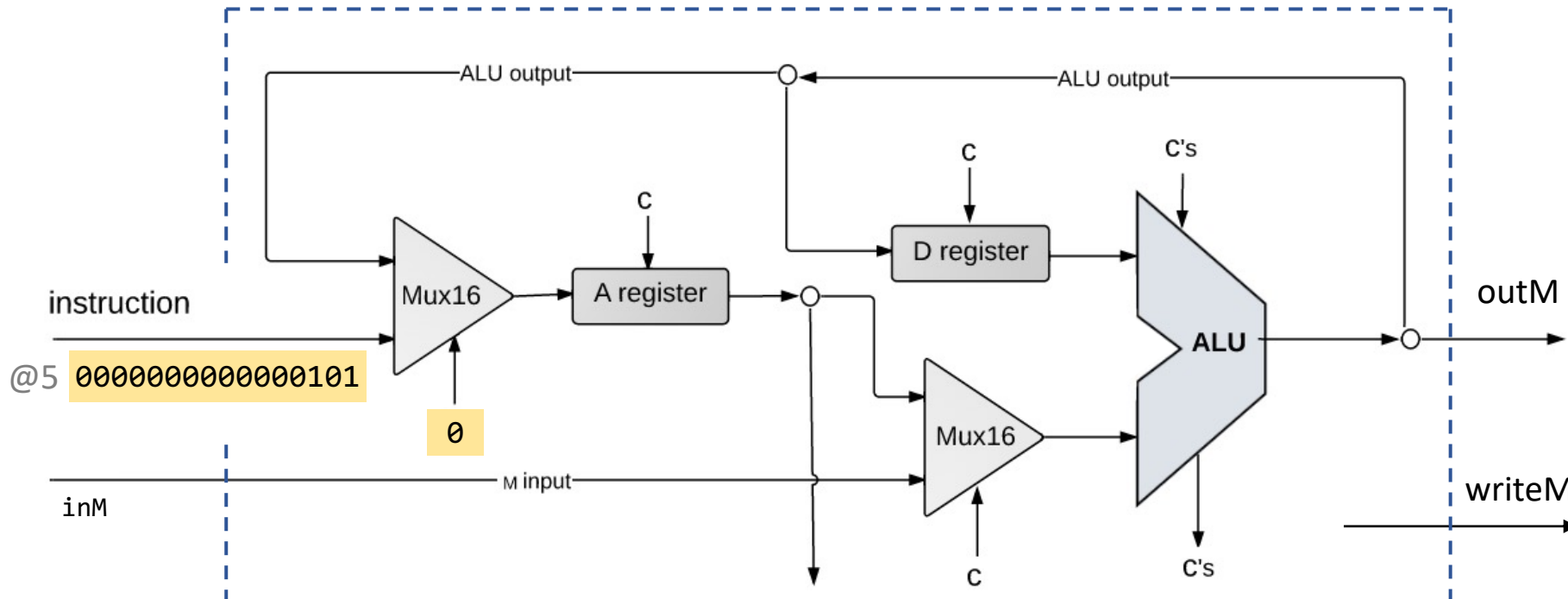
# CPU implementation: Instruction handling




## Handling A-instructions

Routes the instruction's MSB (op-code) to the Mux16 control bit


**Result: A-register  $\leftarrow$  instruction (value)**

(Exactly what the `@xxx` instruction specifies: “set A to `xxx`”)
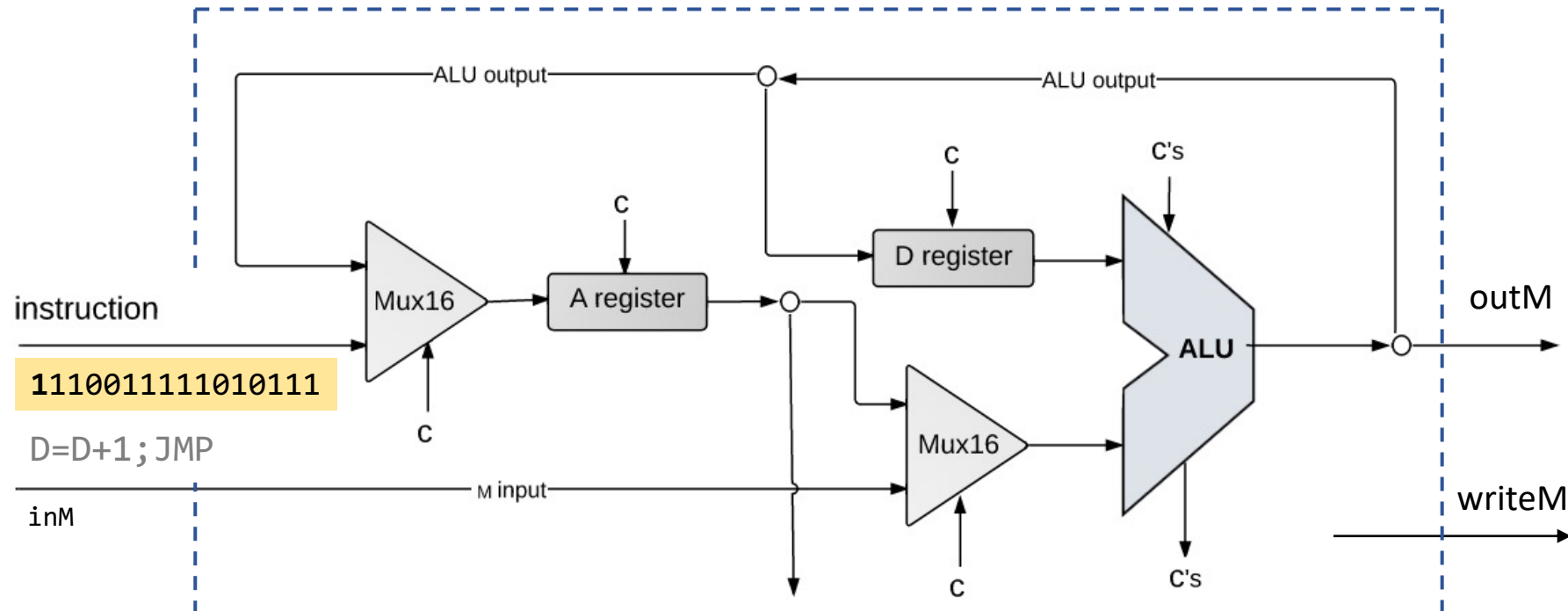
# CPU implementation: Instruction handling


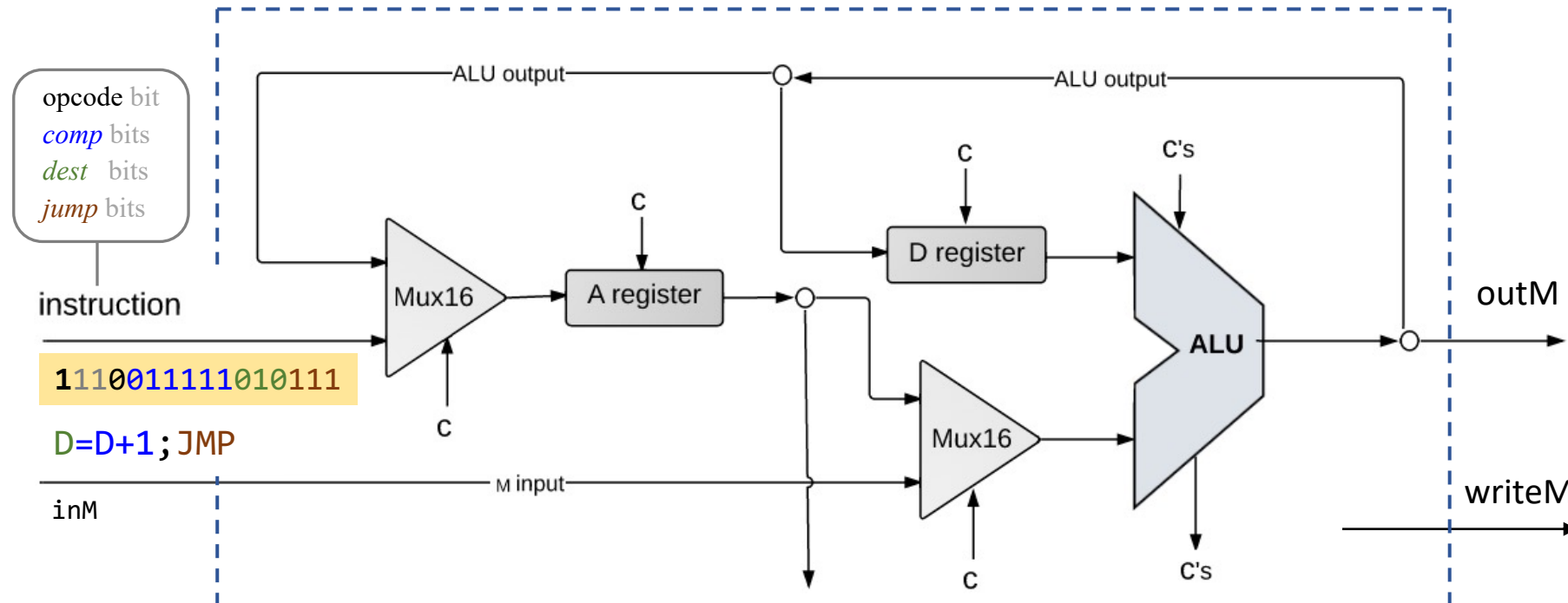
# CPU implementation: Instruction handling




## Handling C-instructions

Each instruction field (*opcode*, *comp* bits, *dest* bits, and *jump* bits) is handled separately

Each group of bits is used to "tell" a CPU chip-part what to do

Taken together, the chip-parts end up executing the instruction.
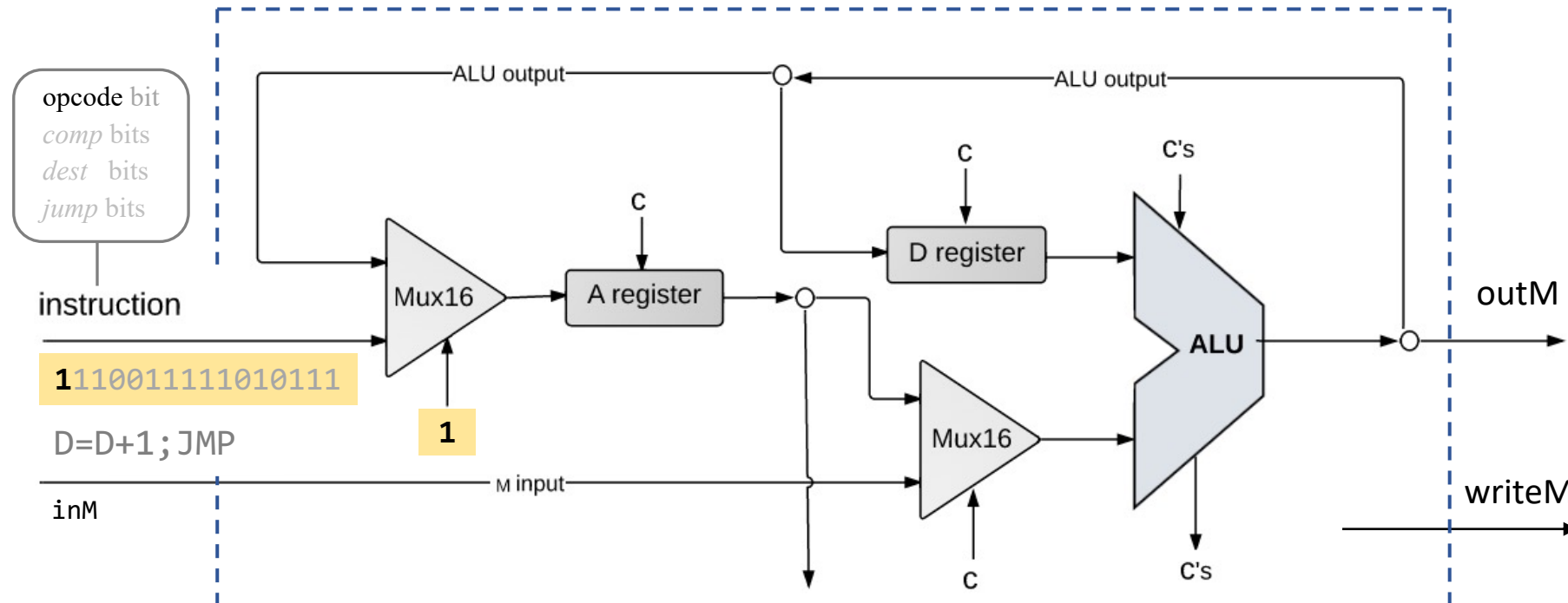
# CPU implementation: Instruction handling




Handling C-instructions (the *opcode* bit):

Routes the instruction's MSB to the Mux16

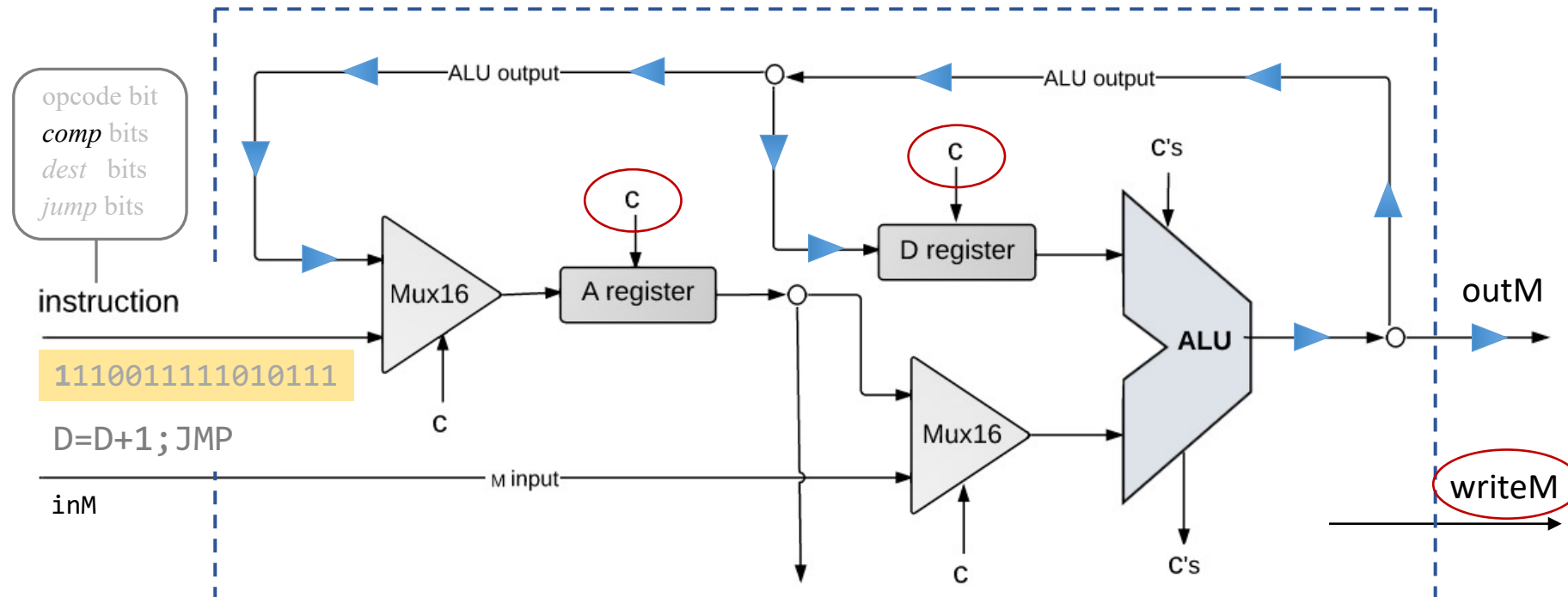
**Result: Prepares the A register to get the ALU output.**





ALU output:

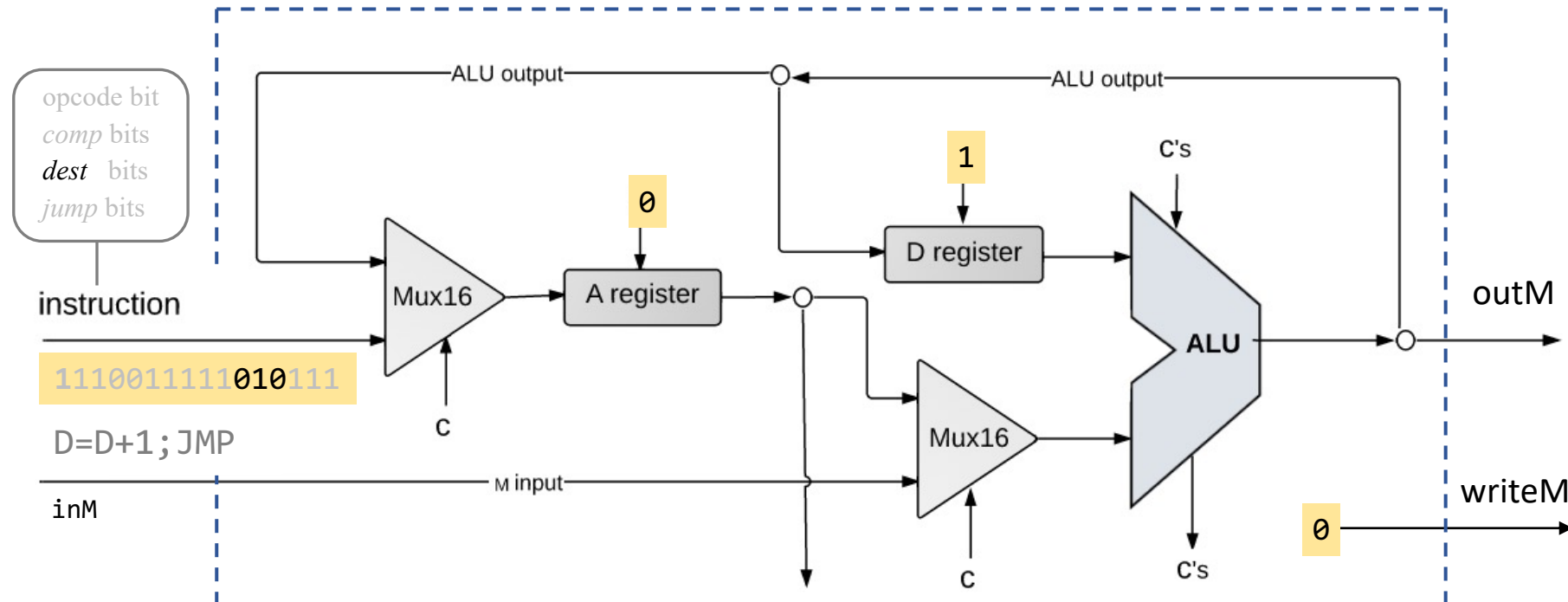- Result of ALU calculation
- Fed simultaneously to D-register, A-register, data memory
- All enabled/disabled by control bits




### Handling C-instructions (the *destination* bits)

Routes the instruction's d-bits to the control (load) bits of the A-register, D-register, and to the writeM bit

**Result: Only the enabled destinations get the ALU output**


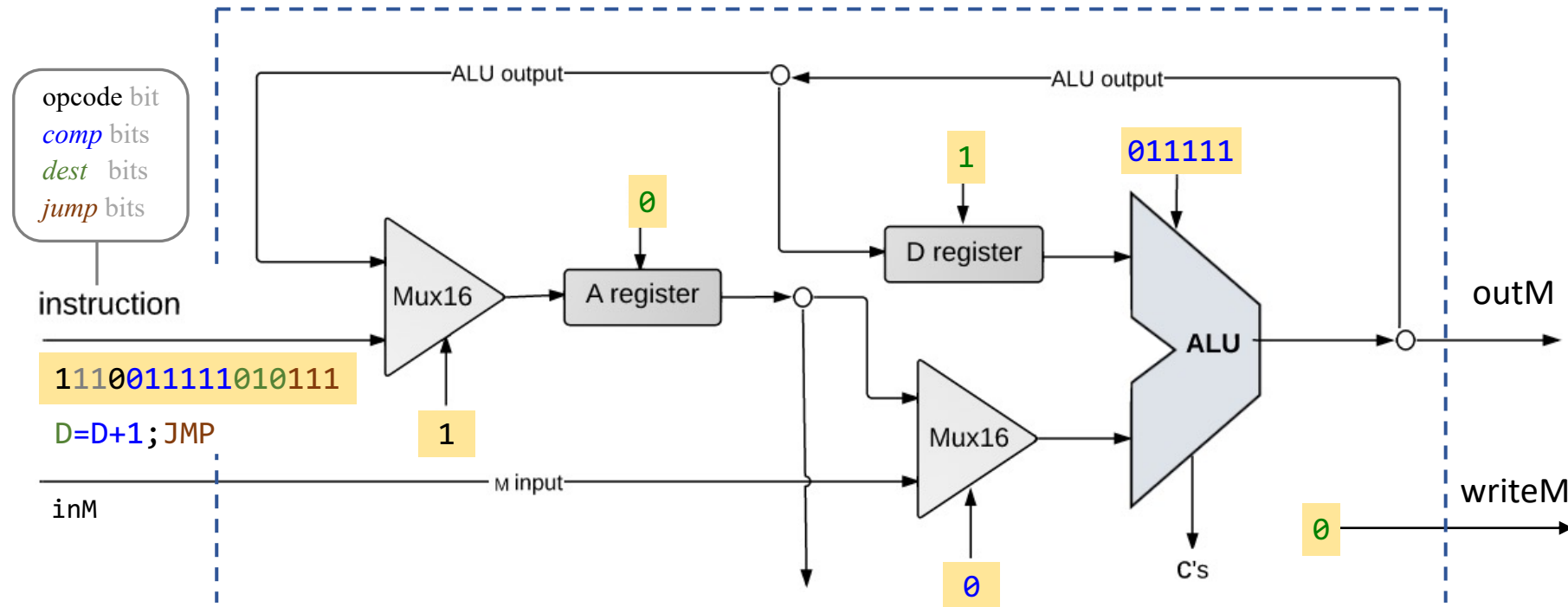
# CPU implementation: Instruction handling



## Handling C-instructions (recap)

- ✓ Executes *dest* = *comp*
- ➔ Figures out which instruction to execute next

# CPU implementation: Control


Symbolic  
syntax:

*dest = comp ; jump*

Binary  
syntax:

1 1 1 a c c c c c c d d d j1 j2 j3

<i>jump</i>	j1	j2	j3	<i>condition</i>
null	0	0	0	no jump
JGT	0	0	1	if (ALU out > 0) jump
JEQ	0	1	0	if (ALU out = 0) jump
JGE	0	1	1	if (ALU out ≥ 0) jump
JLT	1	0	0	if (ALU out < 0) jump
JNE	1	0	1	if (ALU out ≠ 0) jump
JLE	1	1	0	if (ALU out ≤ 0) jump
JMP	1	1	1	Unconditional jump

 


## Jump decision:

$J(j1, j2, j3, zr, ng) = 1$  if *condition* is true,  
0 otherwise


*J* can be computed using gate logic,  
And then help compute the address  
of the next instruction

# CPU implementation: Control

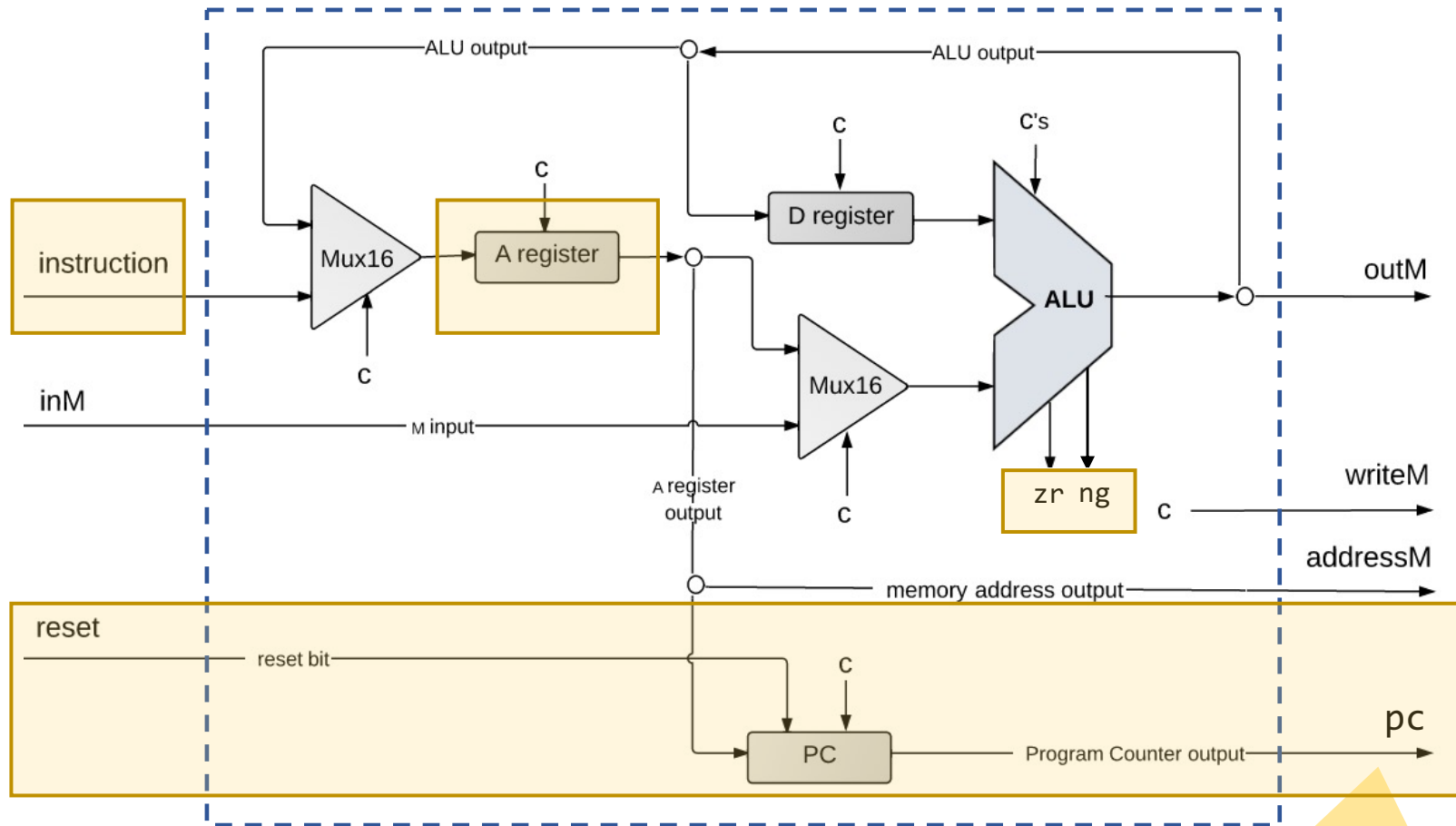

address of next instruction


How to compute it?

 


Outputs the address of the next instruction:

- reset: PC  $\leftarrow \emptyset$
- no jump: PC++
- jump: if (*condition*) PC  $\leftarrow A$  // A contains the address of the  
// jump destination

# CPU implementation: Control

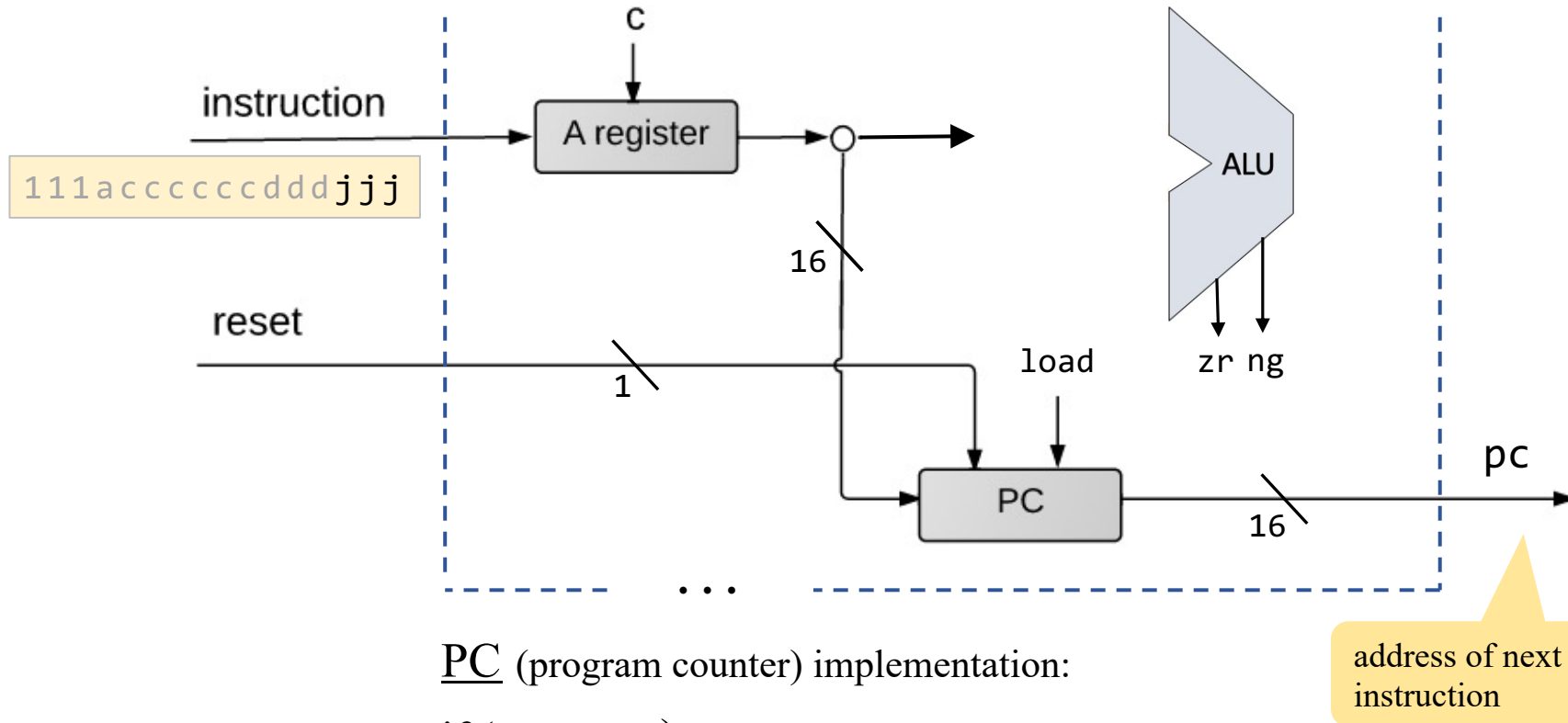

# CPU implementation

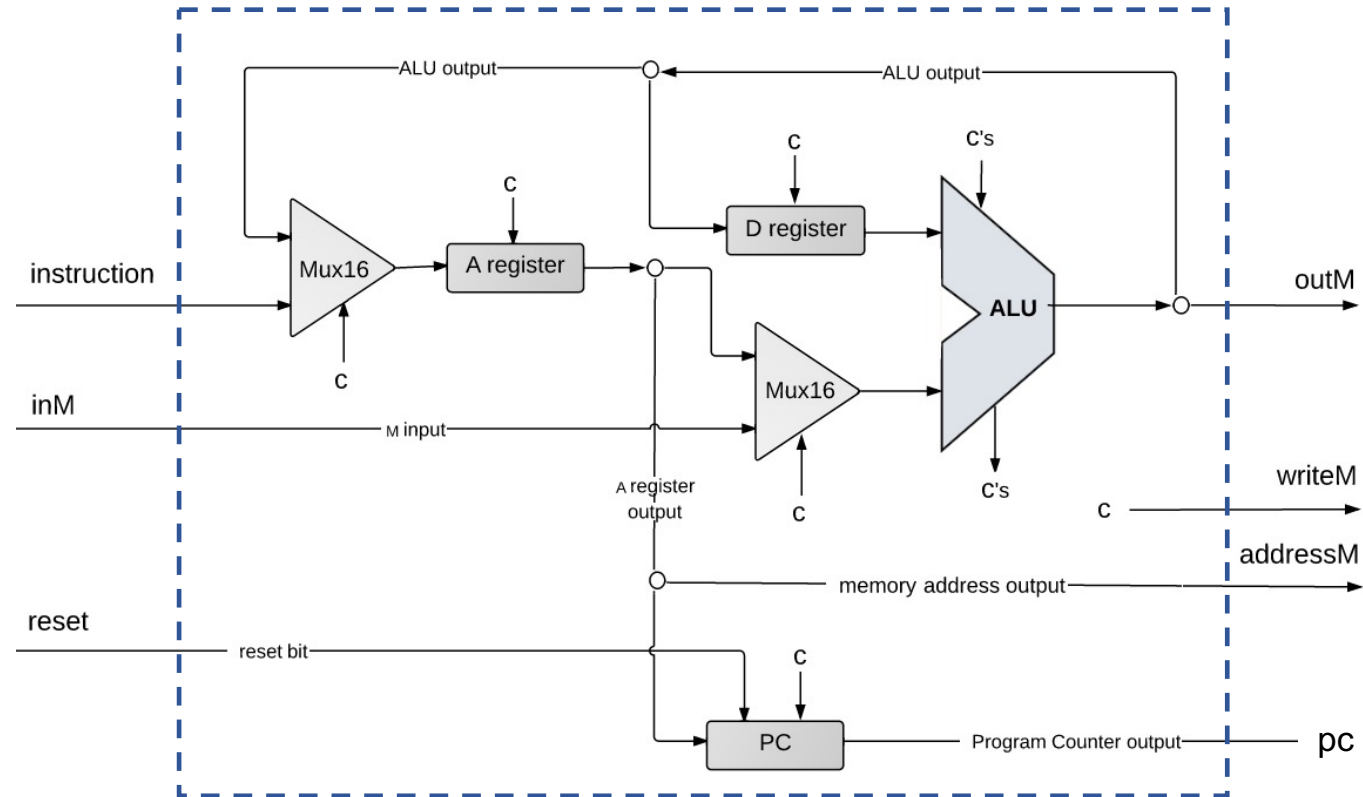

Executes the current instruction



Figures out which instruction to execute next.

# Chapter 5: Computer Architecture

---


- ✓ Basic architecture
- ✓ Fetch-Execute cycle
- ✓ The Hack CPU

➡ Input / output

- Memory
- Computer
- Project 5: Chips
- Project 5: Guidelines




# Hack computer

 

## I/O devices

- ➔ Screen (black and white)
- Keyboard (regular)


# Screen

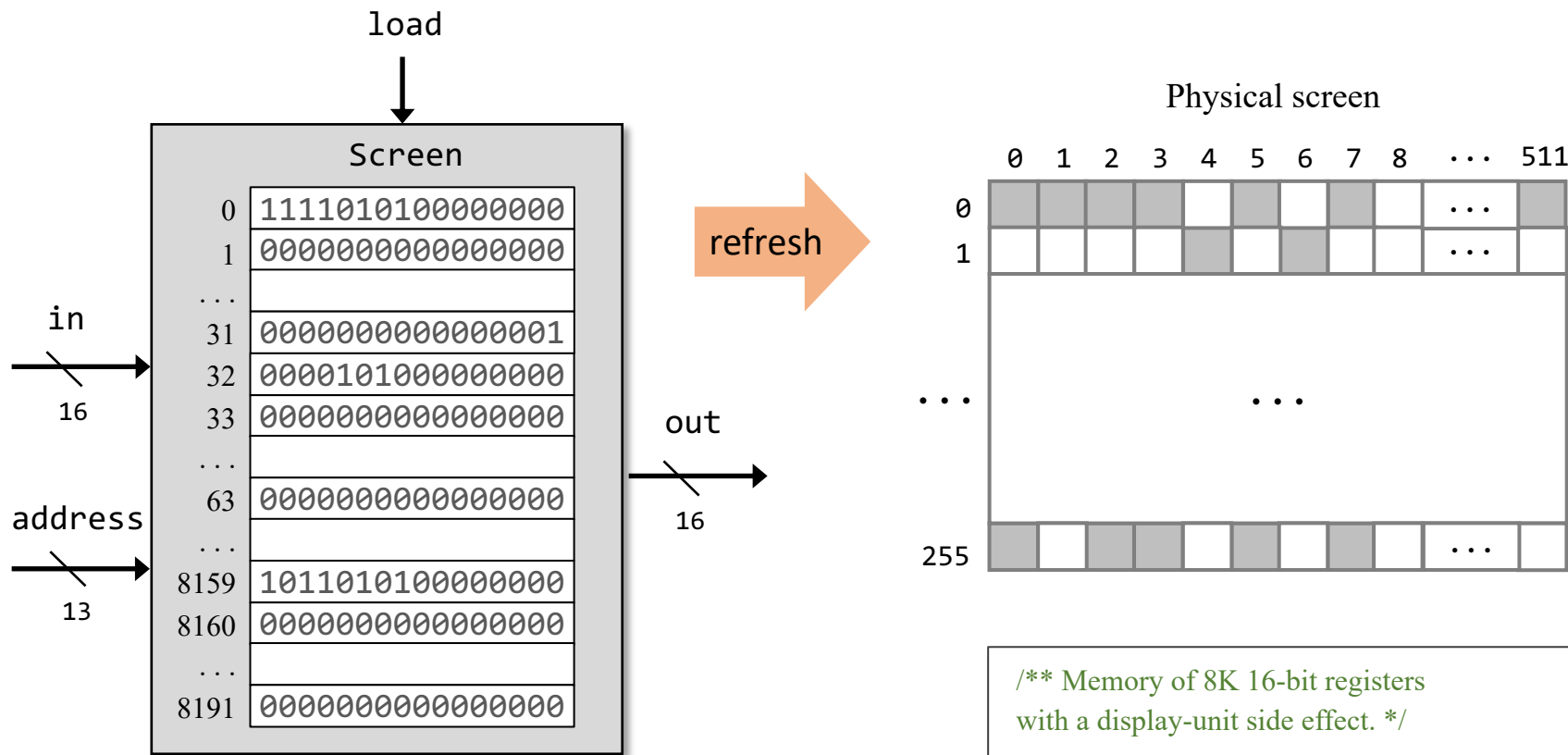

The screen memory map is implemented as an 8K memory chip named Screen

```
/** Memory of 8K 16-bit registers
with a display-unit side effect. */
CHIP Screen {
    IN  address[13], in[16], load;
    OUT out[16];
    BUILTIN Screen;
    CLOCKED in, load;
}
```

# Hack computer

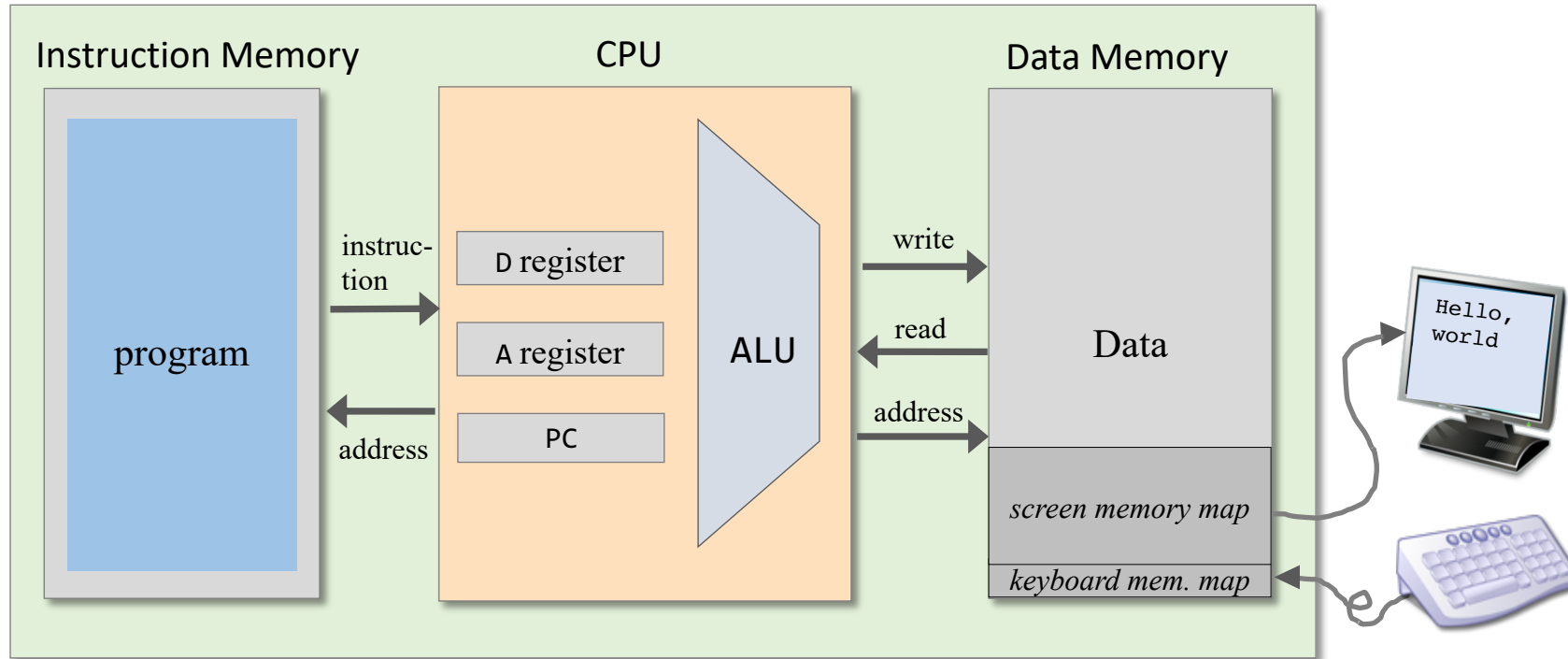


## I/O devices


- Screen (black and white)

➔ Keyboard (regular)

# Keyboard

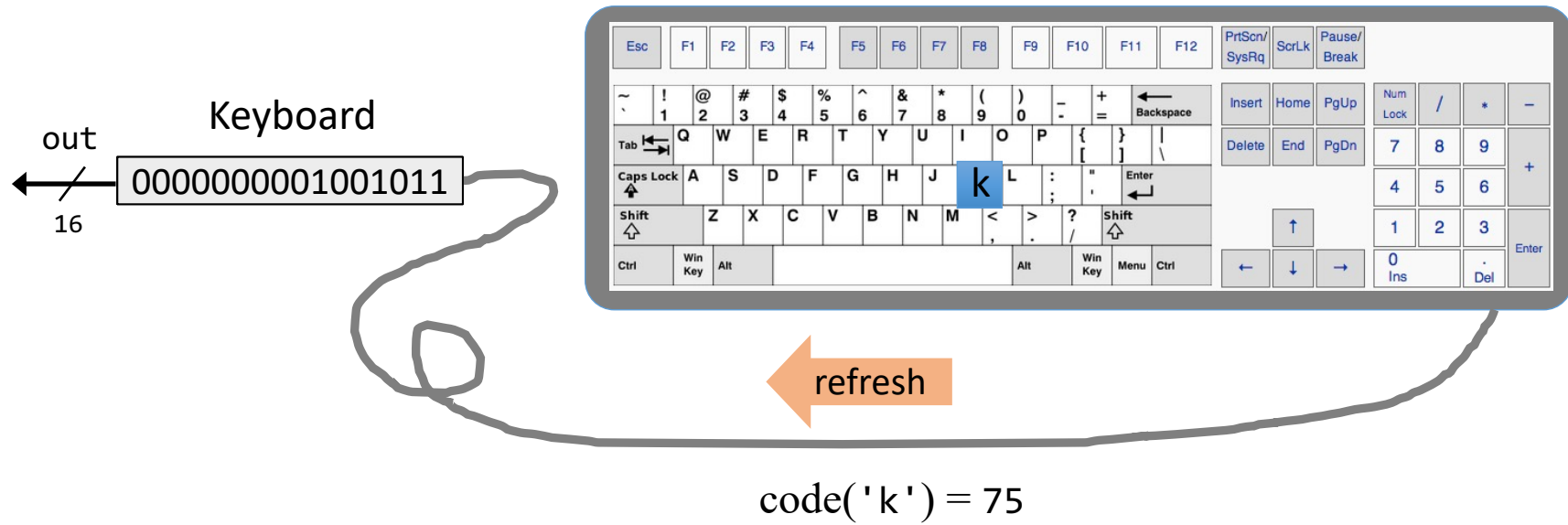

# Keyboard

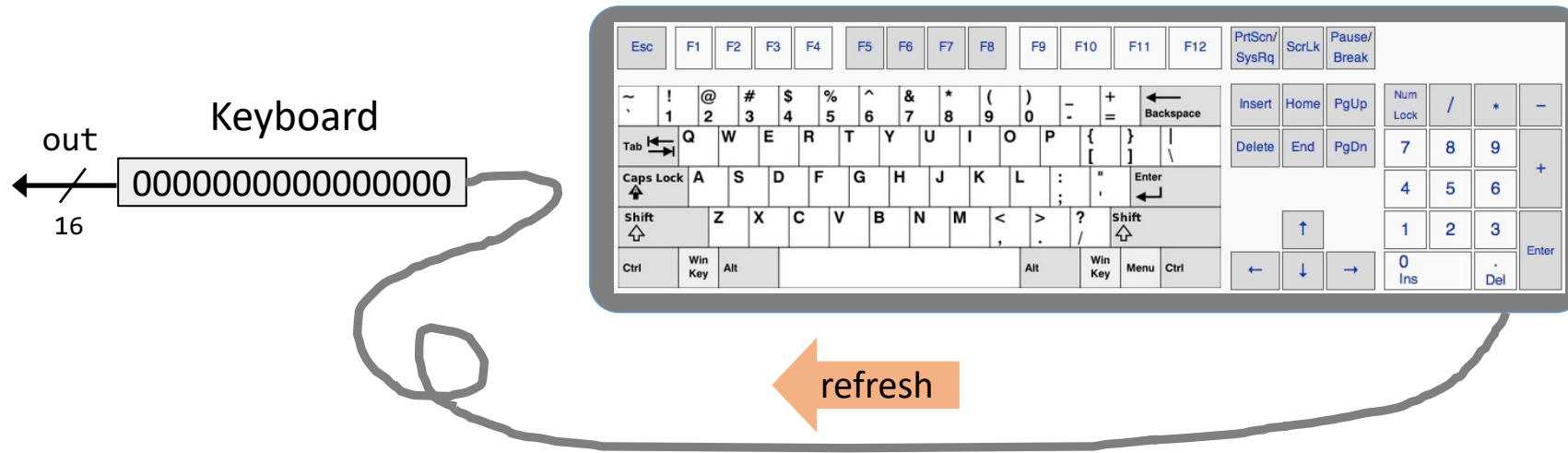

The *keyboard memory map* is implemented as a 16-bit memory register named **Keyboard**

```
/** 16-bit register that outputs the character code of the
    currently pressed keyboard key, or 0 if no key is pressed */
CHIP Keyboard {
    OUT
    out[16];
    BUILTIN Keyboard;
}
```

# The Hack character set

key	code
(space)	32
!	33
“	34
#	35
\$	36
%	37
&	38
‘	39
(	40
)	41
*	42
+	43
,	44
-	45
.	46
/	47

key	code
0	48
1	49
...	...
9	57

:	58
;	59
<	60
=	61
>	62
?	63
@	64

key	code
A	65
B	66
C	...
...	...
Z	90

[	91
/	92
]	93
^	94
_	95
`	96


key	code
a	97
b	98
c	99
...	...
z	122

{	123
	124
}	125
~	126

key	code
newline	128
backspace	129
left arrow	130
up arrow	131
right arrow	132
down arrow	133
home	134
end	135
Page up	136
Page down	137
insert	138
delete	139
esc	140
f1	141
...	...
f12	152

(Subset of Unicode)

# Hack computer

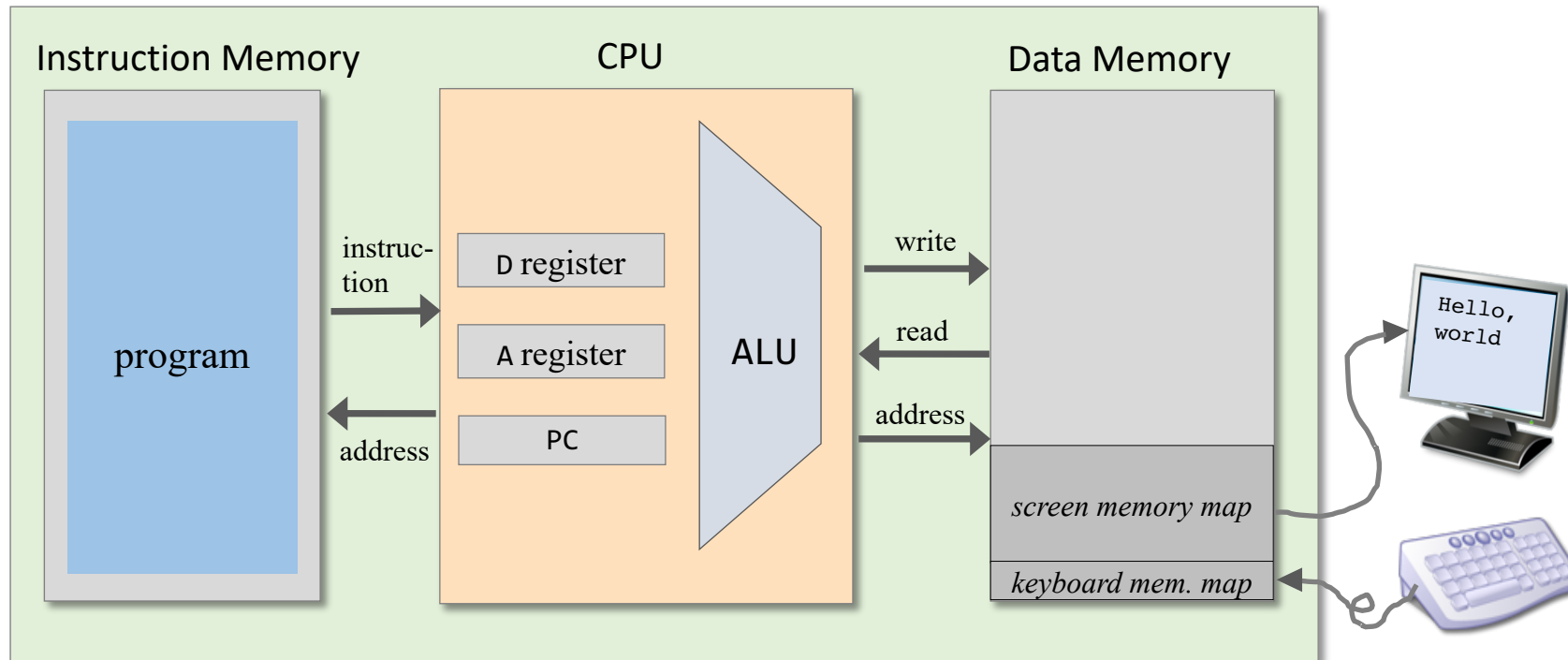

## I/O devices

- ✓ Screen (black and white)
- ✓ Keyboard (regular)

More I/O devices can be added, as needed  
Each requiring a memory map, and an interaction contract  
Managed jointly by the hardware and the OS.

# Chapter 5: Computer Architecture

---

- Basic architecture
- Fetch-Execute cycle
- The Hack CPU
- Input / output




Memory

- Computer
- Project 5: Chips
- Project 5: Guidelines




# Memory

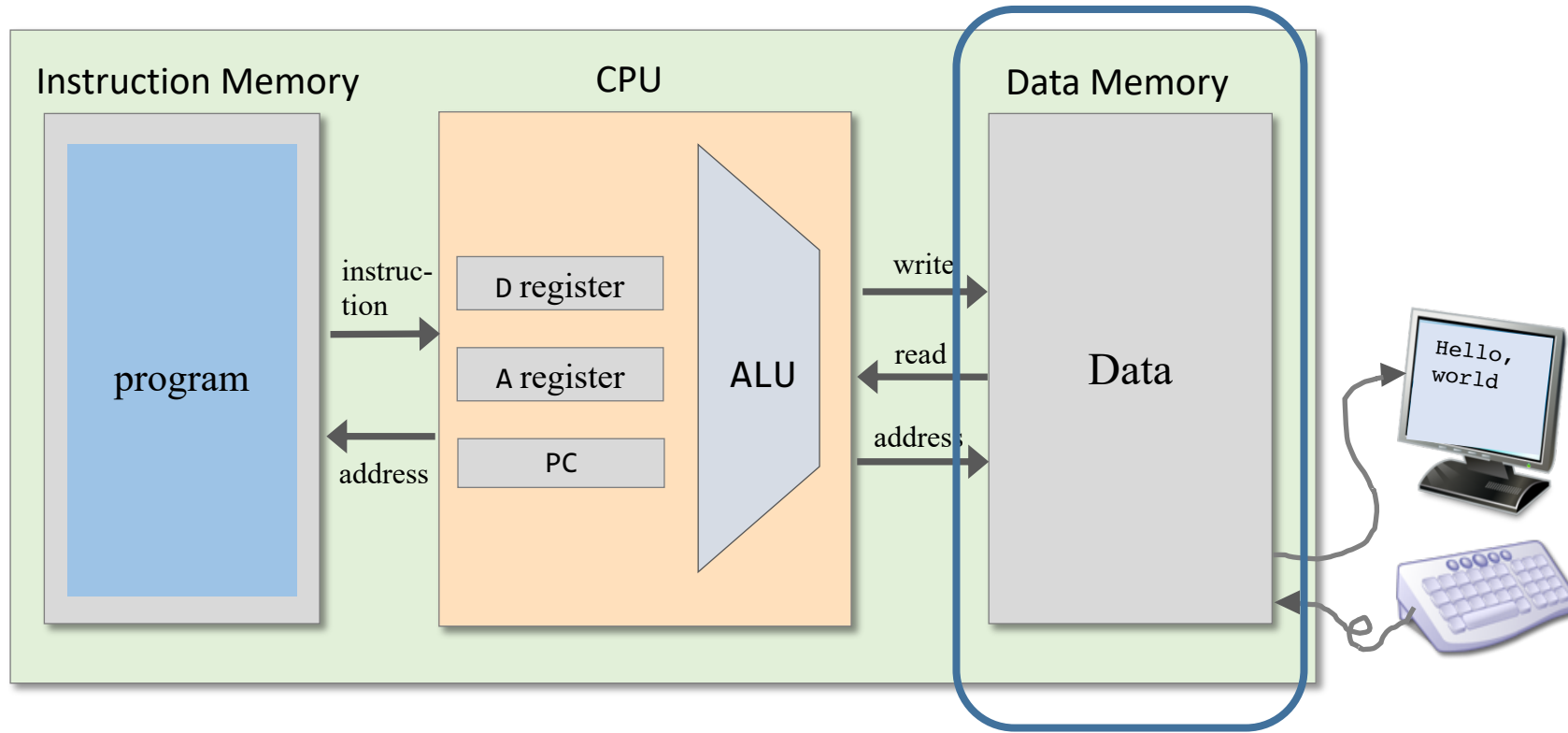

# Memory: Abstraction

---

 

Reading register  $i$ :

$\text{address} \leftarrow i$

Probe out


Setting register  $i$  to  $v$ :

$\text{in} \leftarrow v$

$\text{address} \leftarrow i$

$\text{load} \leftarrow 1$

# Memory: Implementation

 

## Reading register $i$ :

$\text{address} \leftarrow i$

Probe out


## Setting register $i$ to $v$ :

$\text{in} \leftarrow v$

$\text{address} \leftarrow i$

$\text{load} \leftarrow 1$

# Memory: Implementation

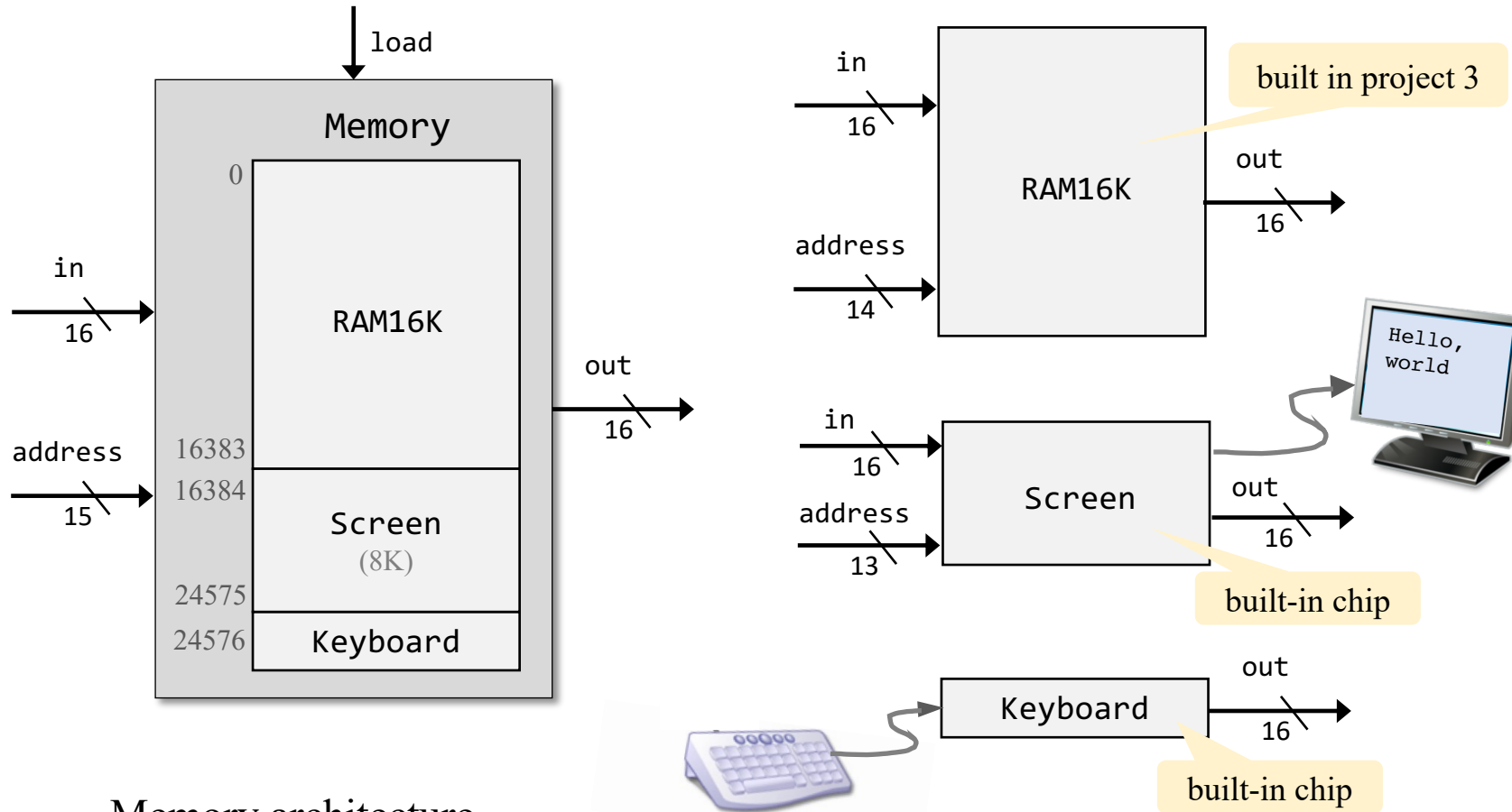


## Memory architecture


- An aggregate of three chip-parts: RAM16K, Screen, Keyboard
- Single address space, 0 to 24576
- Maps the address input onto the corresponding address input of the relevant chip-part.

# Instruction memory

---

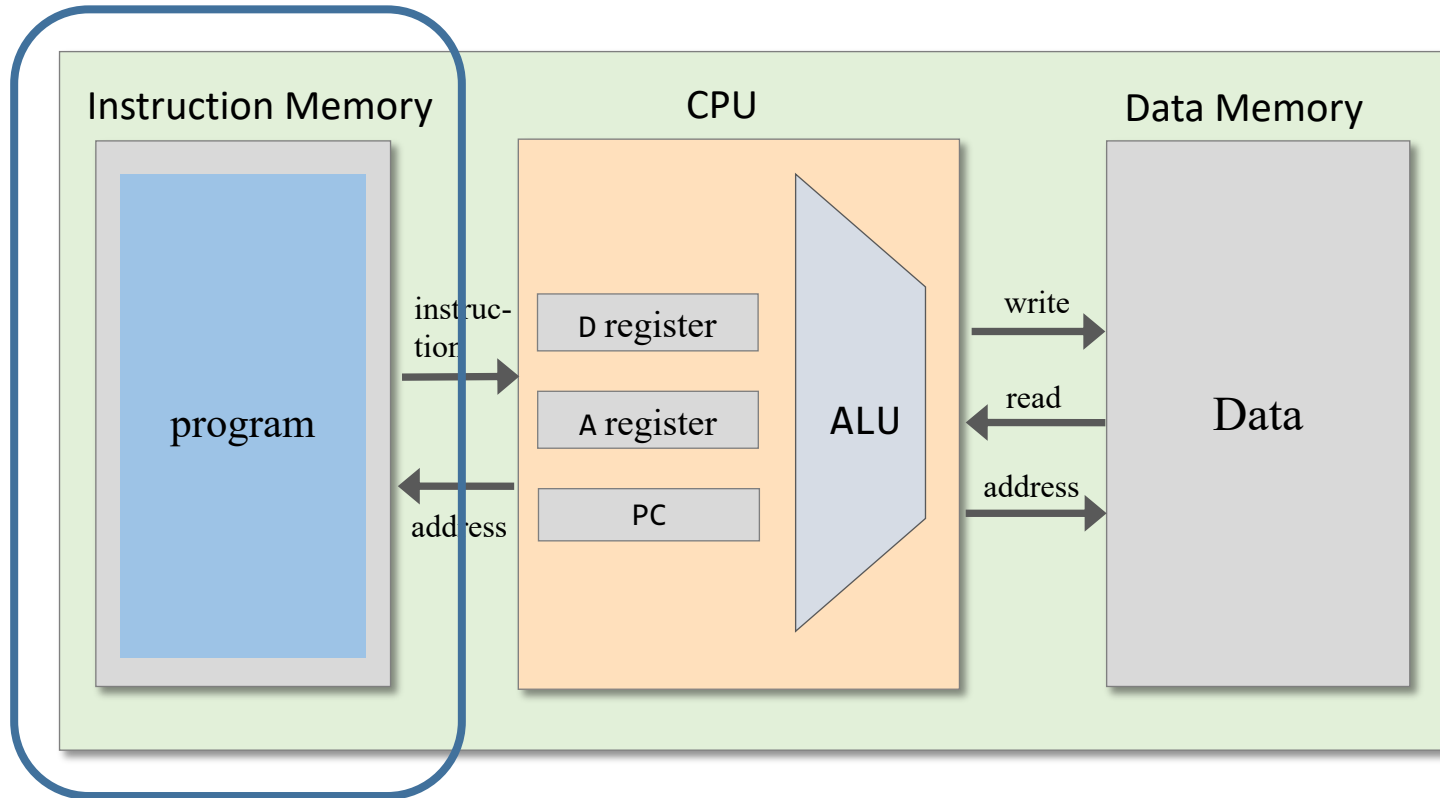

# Instruction memory

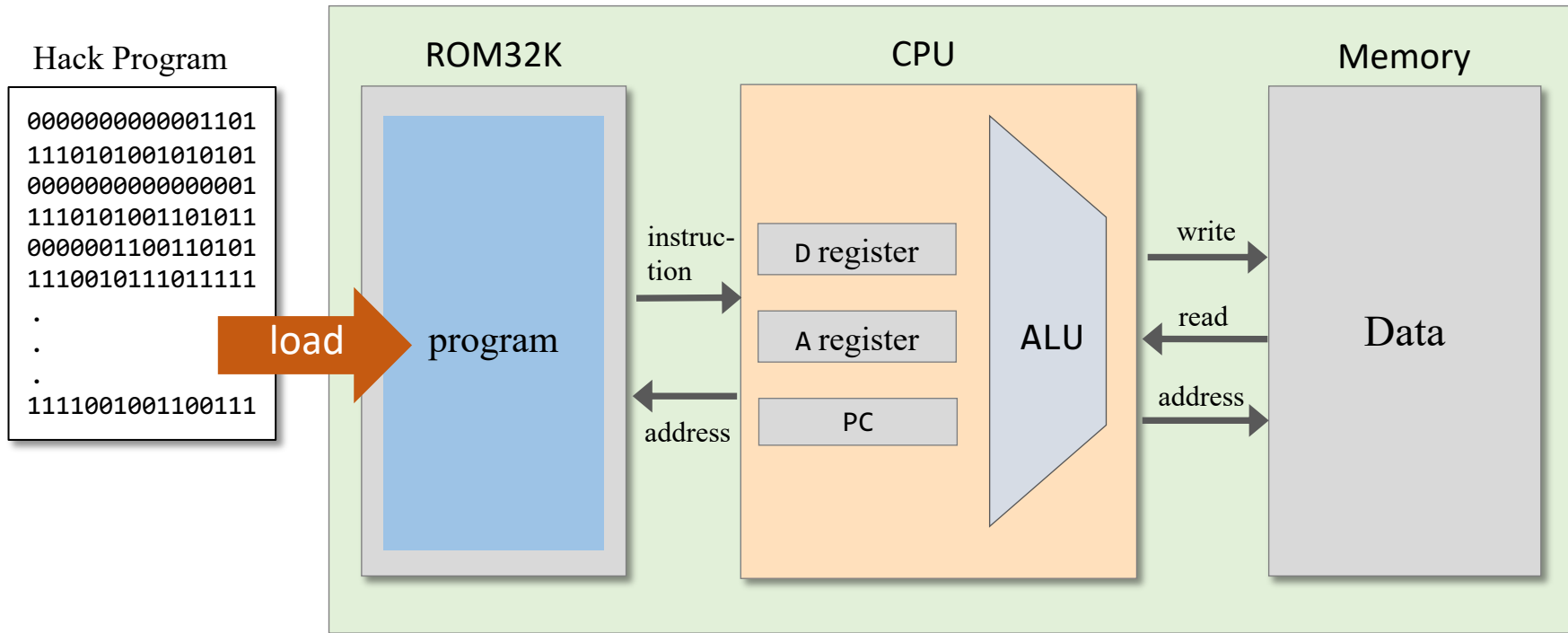


## Hardware implementation

Plug-and-play ROM chip,  
named ROM32K  
(pre-loaded with a program)

```
/** Read-Only memory (ROM),  
    acts as the Hack computer instruction memory. */  
CHIP ROM32K {  
    IN  address[15];  
    OUT out[16];  
    BUILTIN ROM32K;  
}
```

# Instruction memory

 

## Hardware implementation

Plug-and-play ROM chip,  
named ROM32K  
(pre-loaded with a program)

## Hardware simulation

- Programs are stored in text files;
- The simulator software features a *load-program* service.

# Chapter 5: Computer Architecture

---

- Basic architecture
- Fetch-Execute cycle
- The Hack CPU
- Input / output

✓ Memory


➔ Computer

- Project 5: Chips
- Project 5: Guidelines



# Hack computer architecture

---

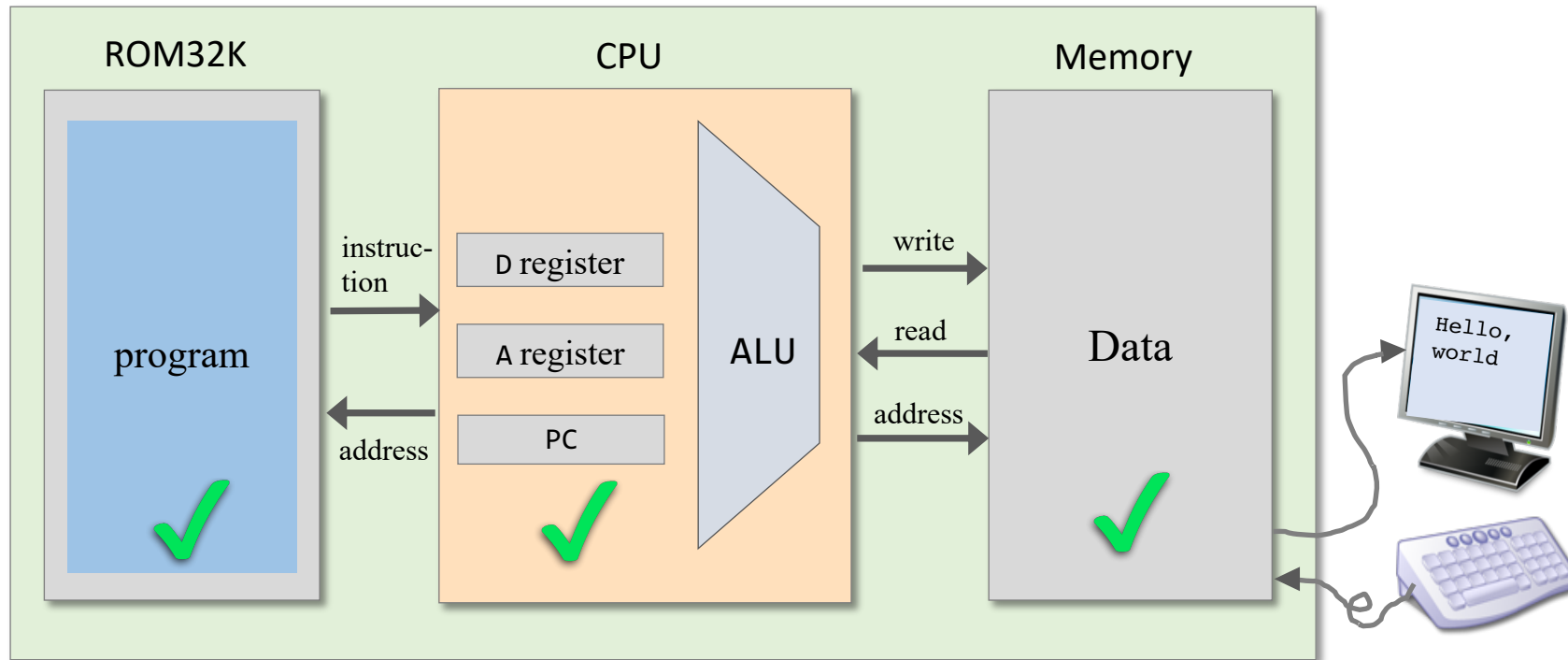

## Remaining challenge

Integrate into a single Computer chip

# Computer abstraction

---

## Assumption:

The computer is loaded with a program written in the Hack machine language

## Computer abstraction:

if ( $\text{reset} == 1$ ), executes the *first* instruction in the stored program

if ( $\text{reset} == 0$ ), executes the *next* instruction in the stored program

↑  
reset

like pushing and releasing a button




## To execute the stored program:


set  $\text{reset} \leftarrow 1$ , then

set  $\text{reset} \leftarrow 0$


# Computer implementation

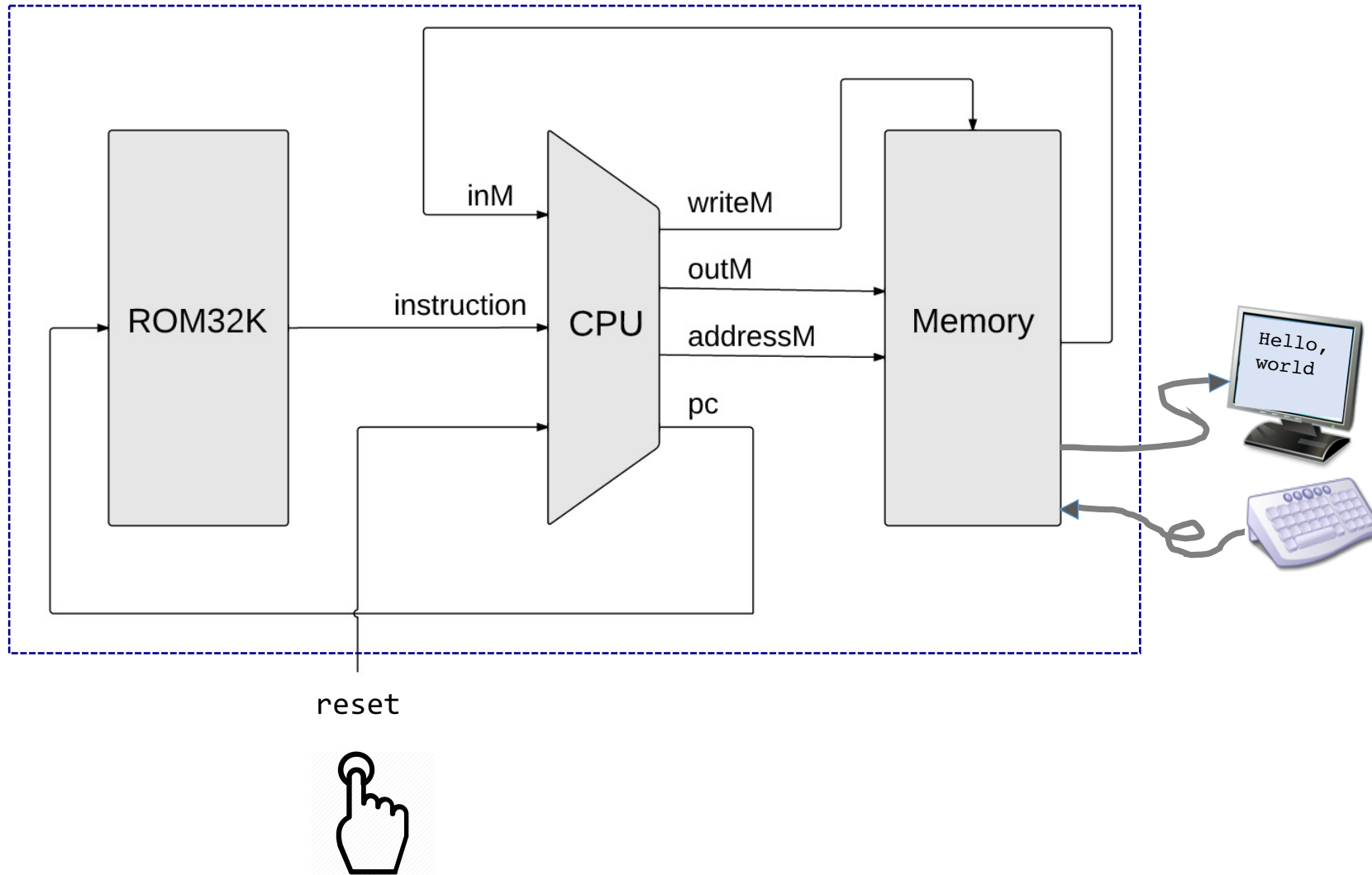

# Computer implementation

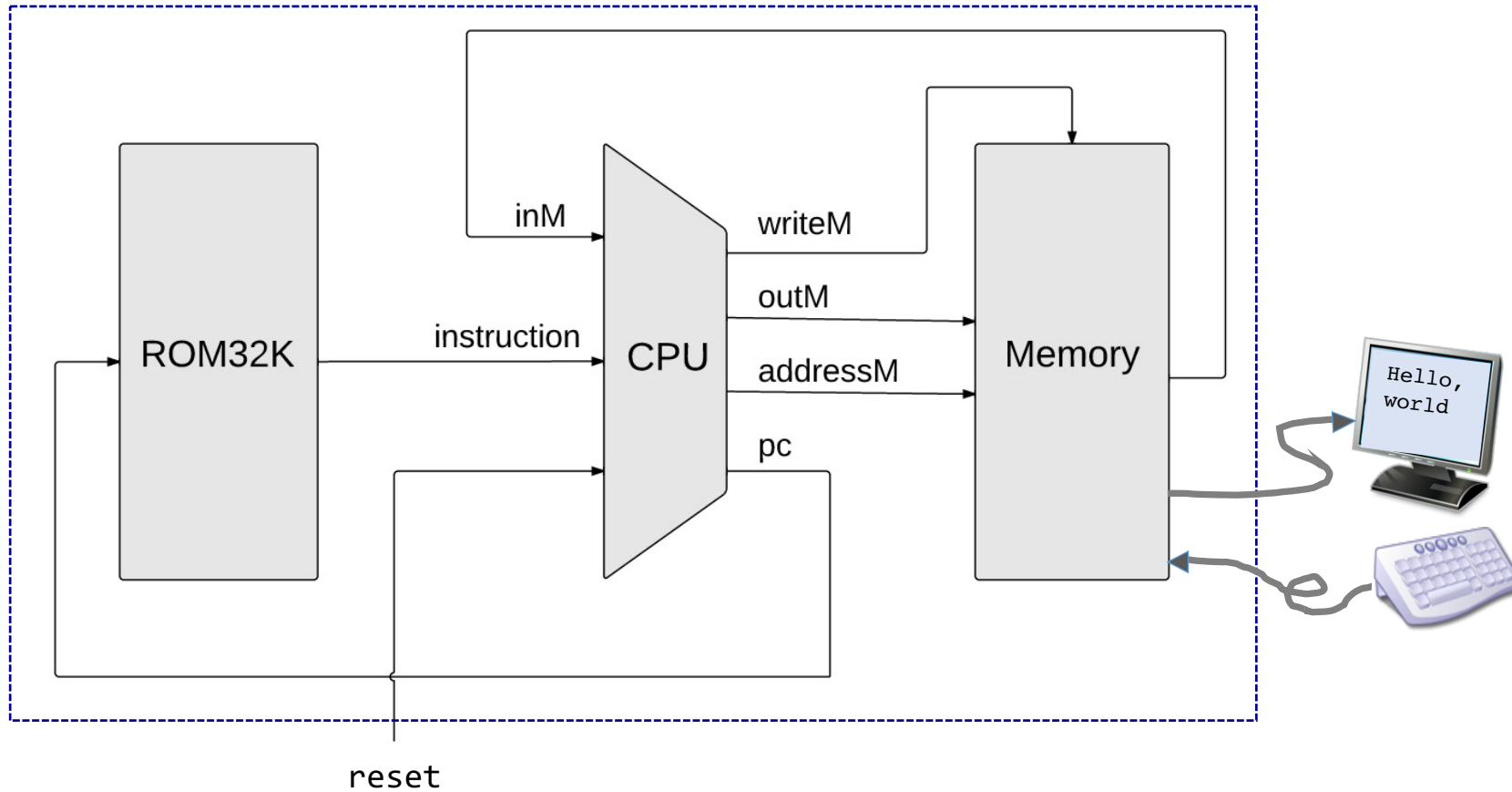

# Computer implementation

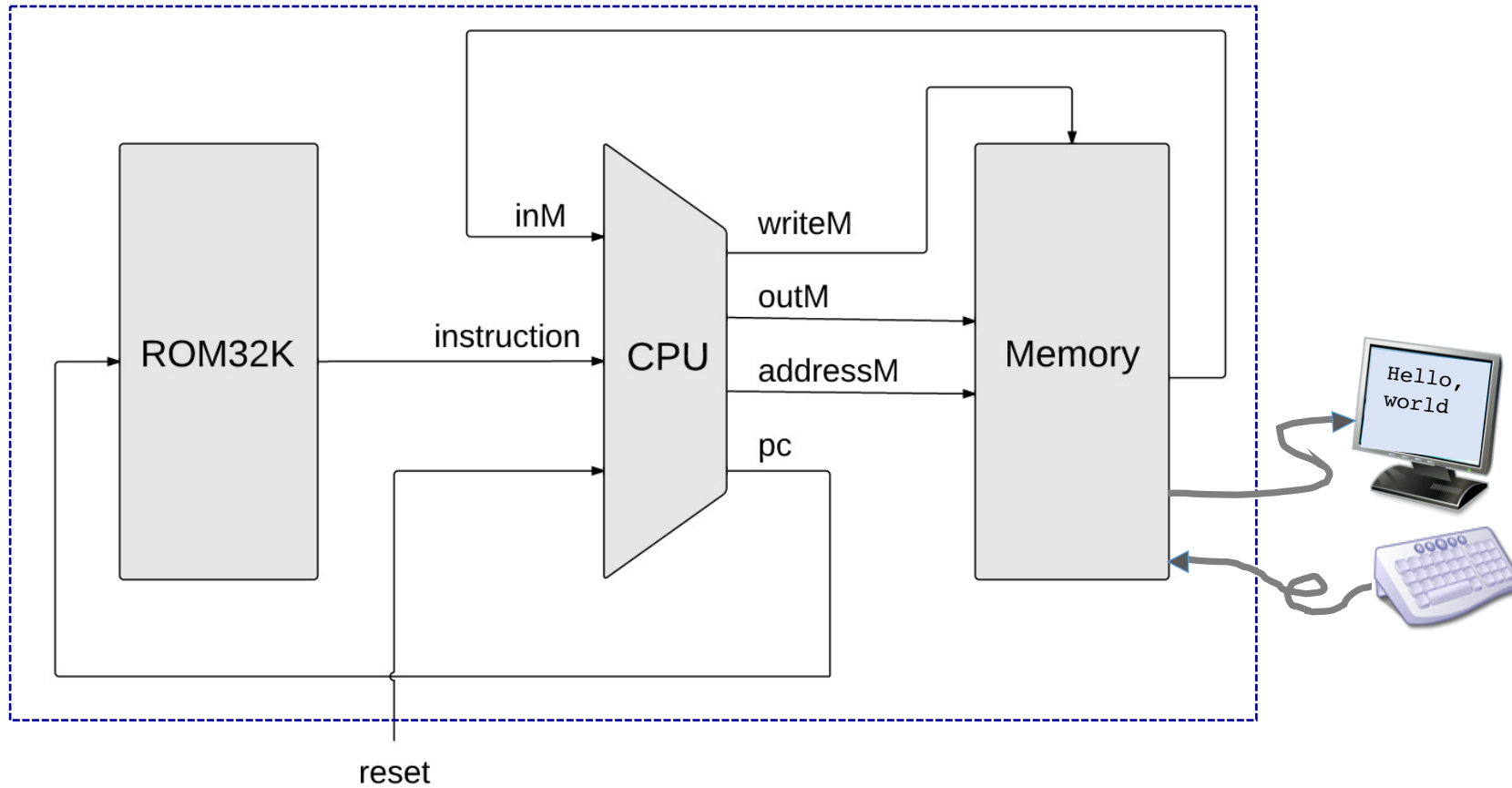

*“Make everything as simple as possible, but no simpler.”*

– Albert Einstein

# Chapter 5: Computer Architecture

---

- Basic architecture
- Fetch-Execute cycle
- The Hack CPU
- Input / output

✓ Memory


✓ Computer

➡ Project 5: Chips


- Project 5: Guidelines

# Hack computer

---

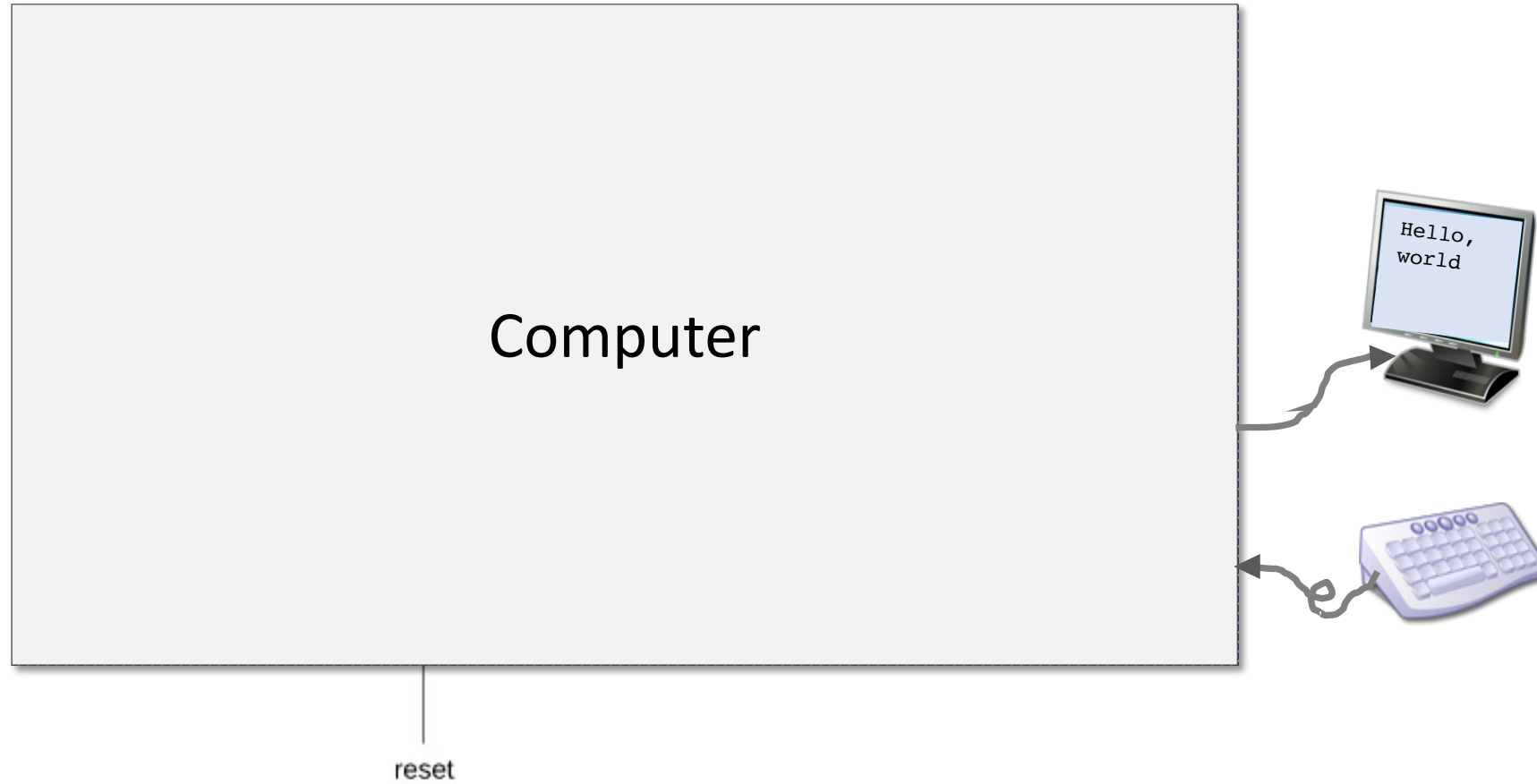


# Hack computer

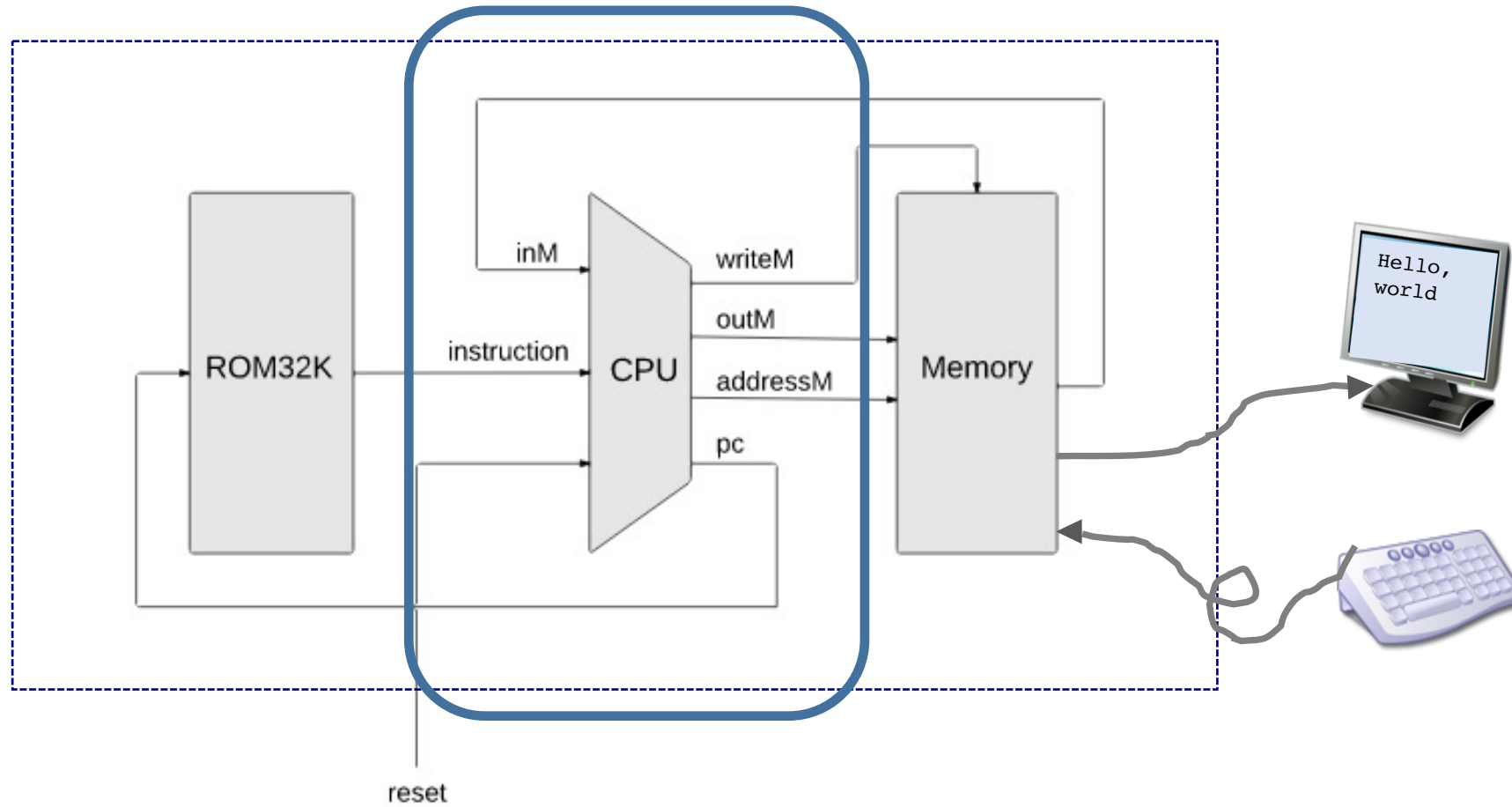



 
# CPU

```
/** Central Processing unit.  
    Executes instructions written in Hack machine language.  
CHIP CPU {  
    IN  
        inM[16],           // Value of M (RAM[A])  
        instruction[16],   // Instruction to execute  
        reset;             // Signals whether to execute the first instruction  
                           // (reset==1) or next instruction (reset == 0)  
  
    OUT  
        outM[16]           // Value to write to the selected RAM register  
        writeM,            // Write to the RAM?  
        addressM[15],      // Address of the selected RAM register  
        pc[15];            // Address of the next instruction  
  
    PARTS:  
        // Put your code here:  
}
```



# CPU implementation

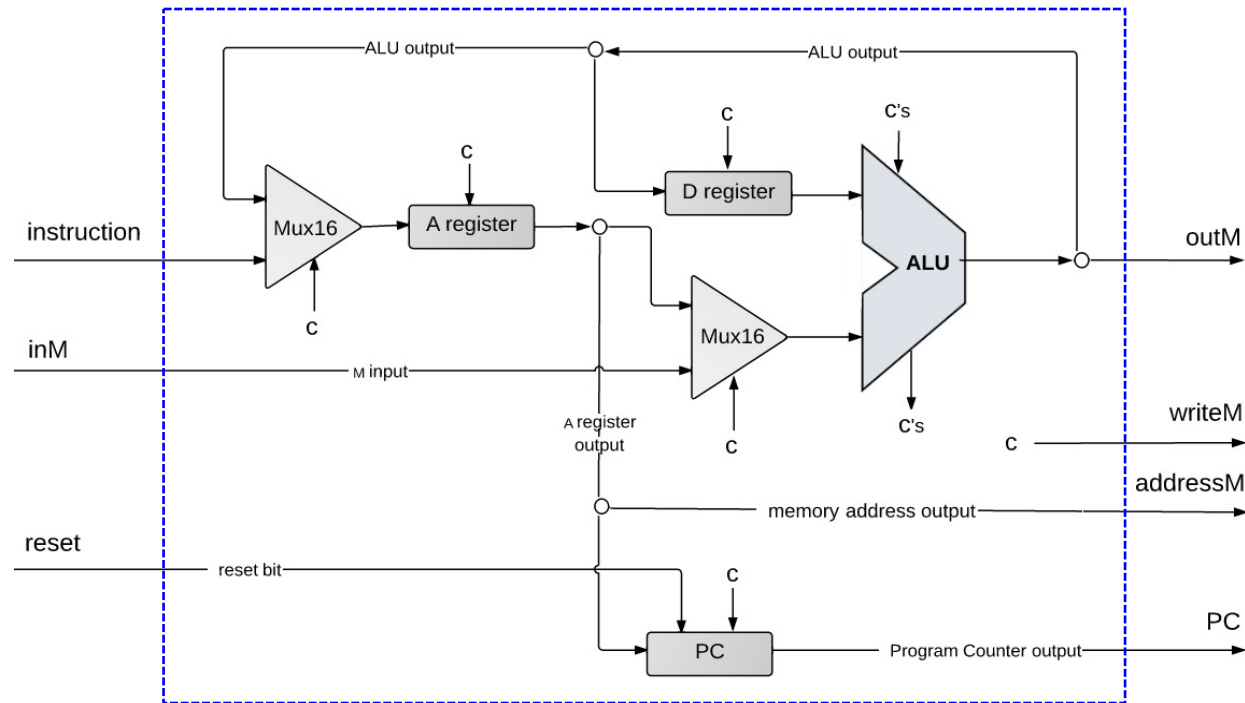

## Chip parts:

Built in  
project 1 and  
project 2


{ Mux16  
ALU  
And, Or, Not ...

ARegister  
DRegister  
PC

Built in project 3

ARegister and Dregister  
are built-in Register chips

# CPU implementation

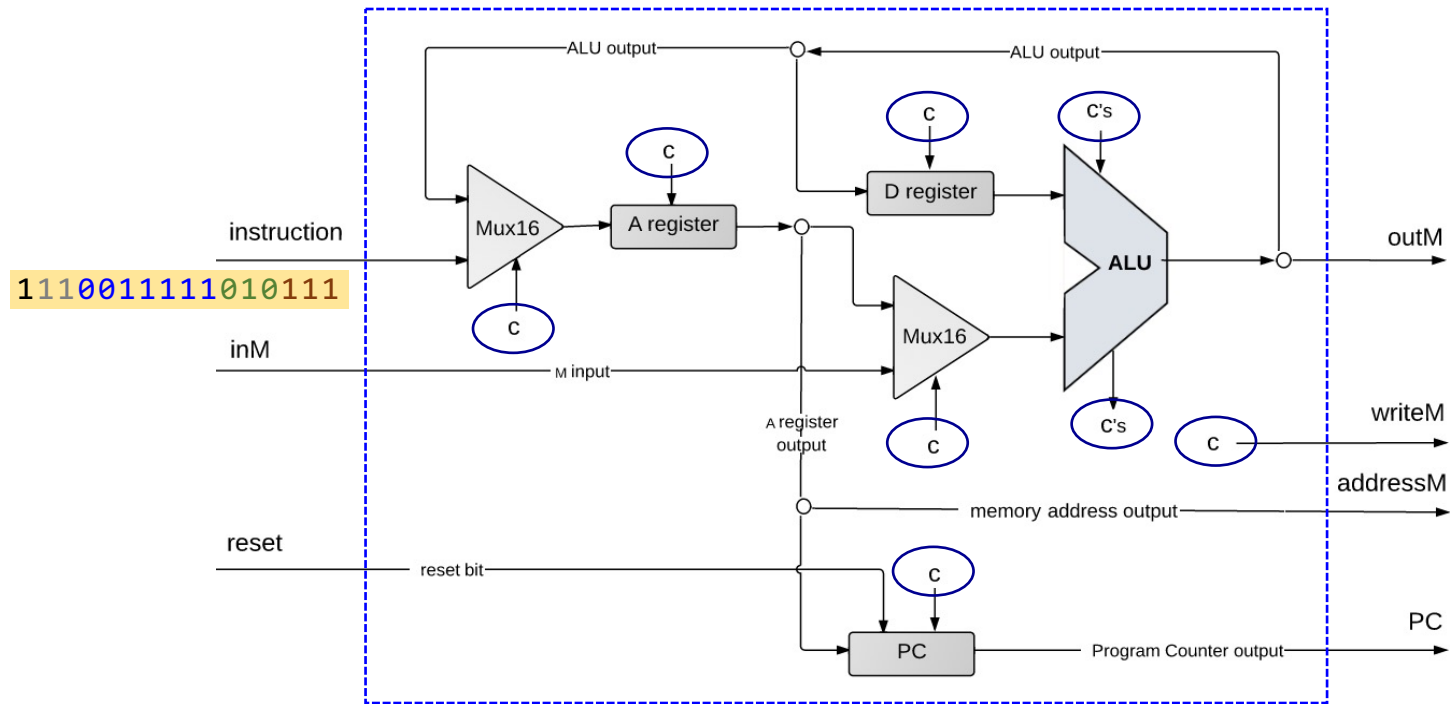


## Implementation

- Use HDL to route instruction bits to chip-parts
- Use gate logic to compute the address of the next instruction


## Tips

- No need for “helper chips”
- Use logic gates and HDL for implementing everything.

# Computer

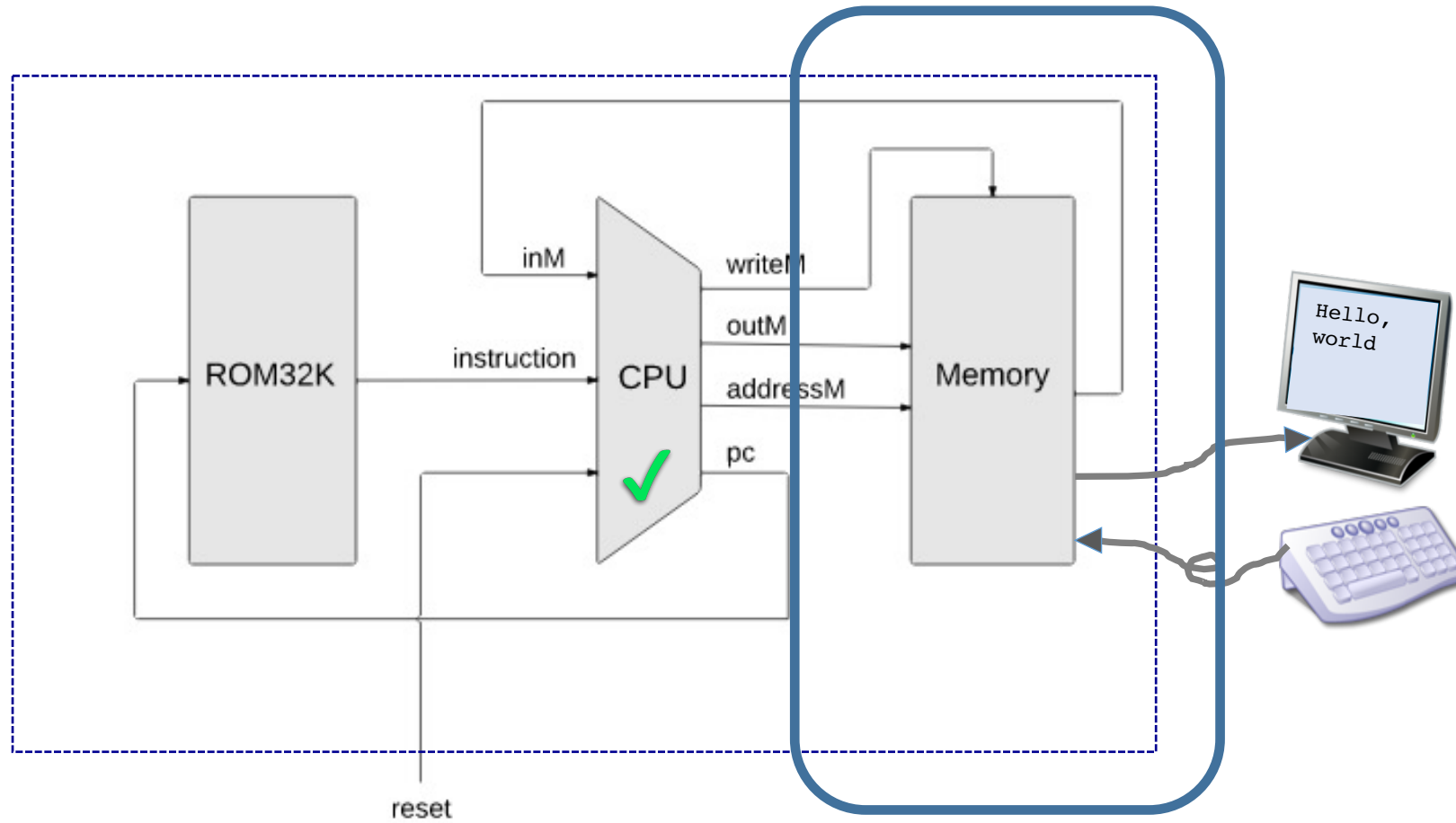

# Memory

 

## Memory.hdl

```
/** Complete address space of the computer's data memory,
    including RAM and memory mapped I/O.

    Outputs the value of the memory location specified by address.


    If (load==1), the in value is loaded into the memory location
    specified by address.

    Address space rules:
    Only the upper 16K+8K+1 words of the memory are used.
    Access to address 0 to 16383 results in accessing the RAM;
    Access to address 16384 to 24575 results in accessing
    the Screen memory map;
    Access to address 24576 results in accessing the Keyboard
    memory map.

    */
CHIP Memory {
    IN    address[15], in[16], load;
    OUT   out[16];

    PARTS:
        // Put your code here.
}
```

# Memory implementation

 

```
/** Memory of 16K 16-bit registers */  
CHIP RAM16K {  
    IN  
        address[14], in[16], load;  
    OUT  
        out[16];  
}
```

built in project 3



```
/** Memory of 8K 16-bit registers  
with a display unit side effect. */  
CHIP Screen {  
    IN  
        address[13], in[16], load;  
    OUT  
        out[16];  
  
    BUILTIN Screen;  
}
```

```
/** 16-bit register with a  
keyboard input side effect */  
CHIP Keyboard {  
    OUT  
        out[16];  
        BUILTIN Keyboard;  
}
```

## Implementation tip:

Use logic gates for mapping the address input on the corresponding address input of the relevant chip-part.

# Instruction memory

 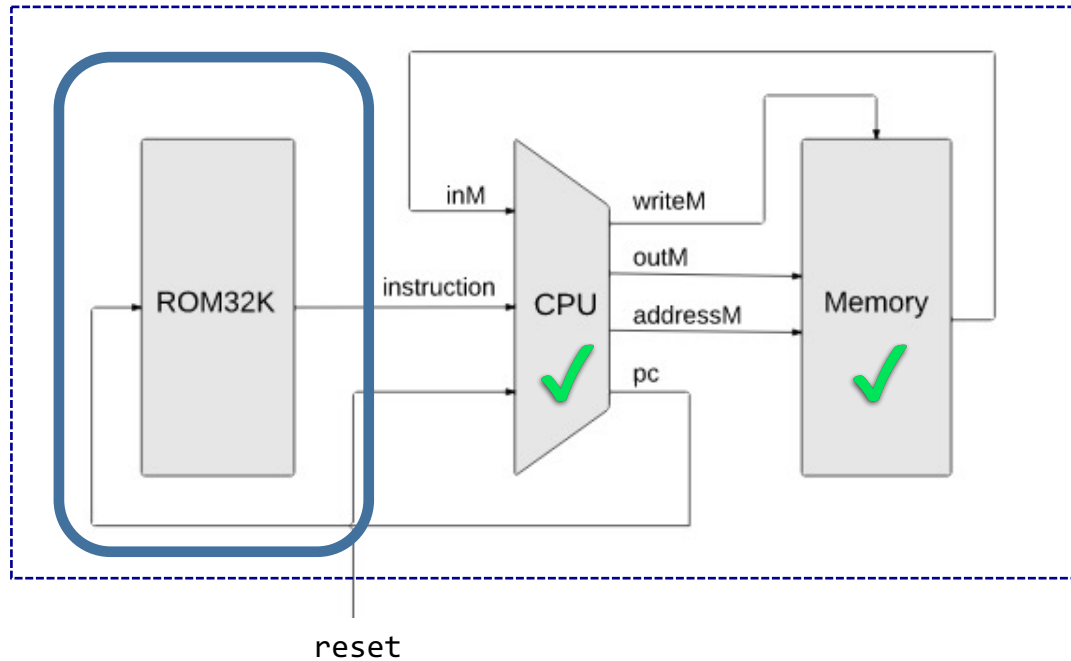


ROM32K.hdl

```
/** Read-Only memory (ROM),  
    acting as the Hack computer instruction memory. */  
CHIP ROM32K {  
    IN  address[15];  
    OUT out[16];  
    BUILTIN ROM32K;  
}
```


# Computer

---

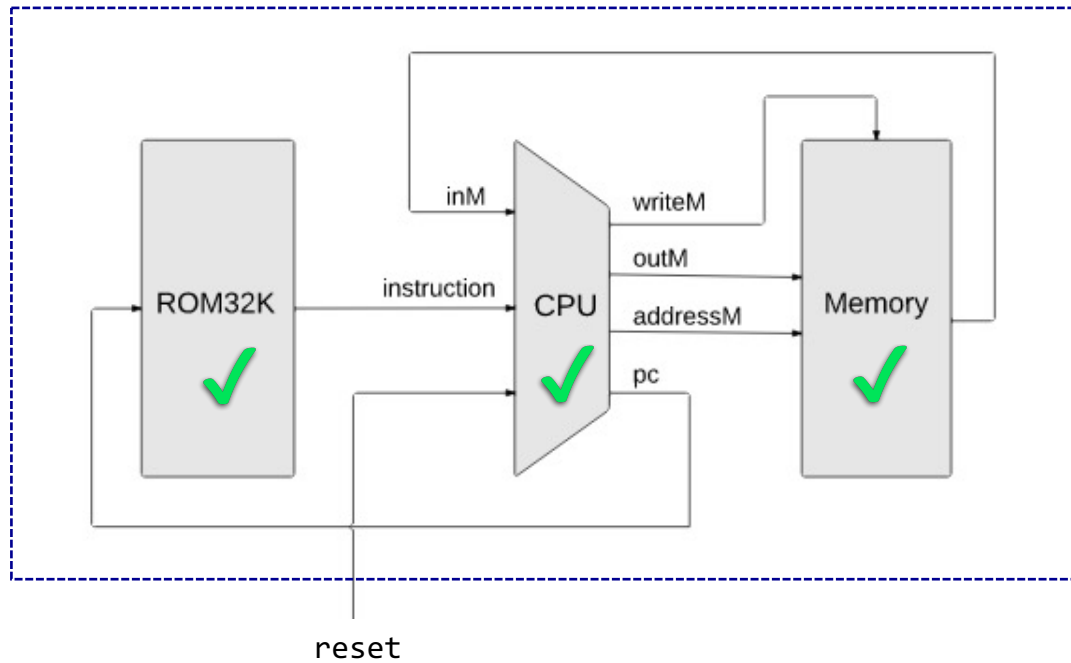



# Computer implementation

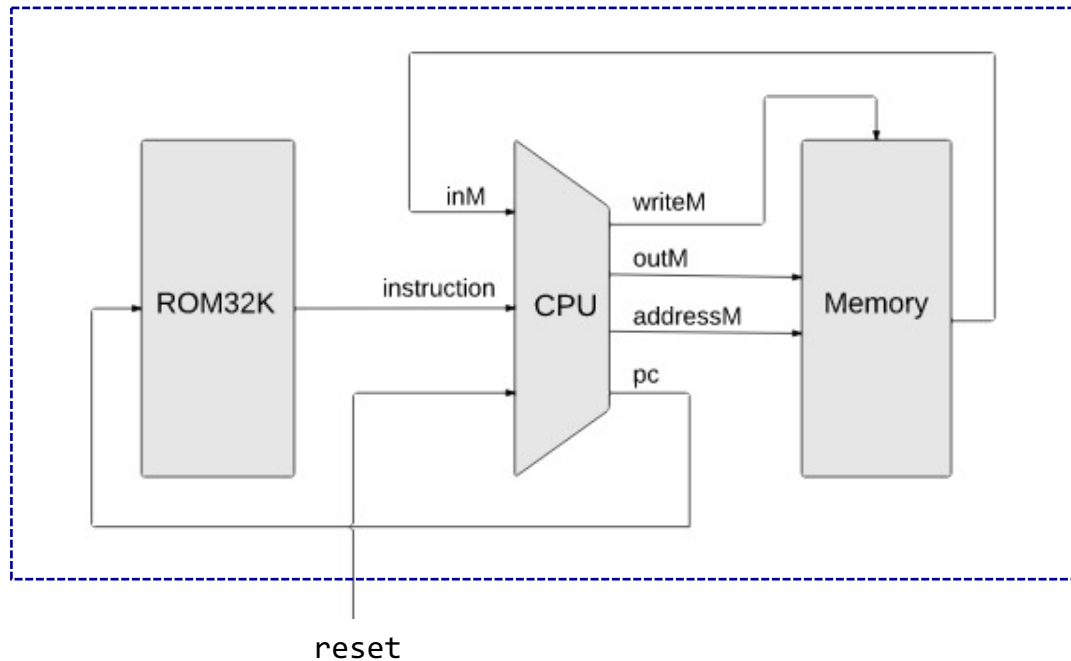

Computer.hdl

```
/** The Hack computer, including CPU, RAM and ROM, loaded with a program.
    When (reset==1), the computer executes the first instruction in the program;
    When (reset==0), the computer executes the next instruction in the program. */
CHIP Computer {
    IN reset;
    PARTS:
        // Put your code here.
}
```

# Chapter 5: Computer Architecture

---

- Basic architecture
- Fetch-Execute cycle
- The Hack CPU
- Input / output

✓ Memory

✓ Computer

✓ Project 5: Chips

➡ Project 5: Guidelines

# Project 5

---

## Build three chips:

- `Memory.hdl`      chip-parts: RAM16K, Screen, Keyboard
- `CPU.hdl`          chip-parts: ARgister, DRegister, PC, ALU, ...
- `Computer.hdl`    chip-parts: CPU, Memory, ROM32K

(All the chip-parts should be built-in chips, except for Memory and CPU)


## Tools

- Text editor
- Hardware simulator

# Testing the computer chip
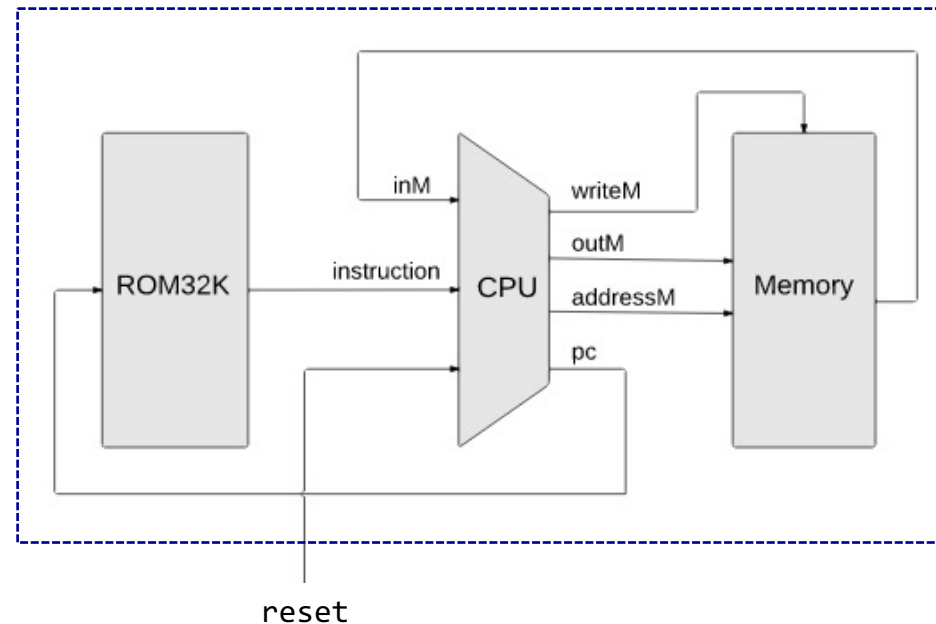
## Testing logic:

- Load Computer.hdl into the hardware simulator
- Load a Hack program into the ROM32K chip-part
- Run the clock enough cycles to execute the program



Computer.hdl

```
/** The Hack computer, including CPU, RAM and ROM, loaded with a program.
 * When (reset==1), the computer executes the first instruction in the program;
 * When (reset==0), the computer executes the next instruction in the program. */
CHIP Computer {
    IN reset;
    PARTS:
        // Put your code here.
}
```

# Testing the computer chip

---

## Testing logic:

- Load `Computer.hdl` into the hardware simulator
- Load a Hack program into the ROM32K chip-part
- Run the clock enough cycles to execute the program

## Test programs


- Add.hack:  
 $\text{RAM}[0] \leftarrow 2 + 3$
- Max.hack:  
 $\text{RAM}[2] \leftarrow \max(\text{RAM}[0], \text{RAM}[1])$
- Rect.hack:  
Draws a rectangle of  $\text{RAM}[0]$  rows of 16 pixels each.

# Testing the computer chip

## Testing logic:

- Load Computer.hdl into the hardware simulator
- Load a Hack program into the ROM32K chip-part
- Run the clock enough cycles to execute the program

## Test programs

- Add.hack:  
RAM[0]  $\leftarrow 2 + 3$
-  Max.hack:  
RAM[2]  $\leftarrow \max(\text{RAM}[0], \text{RAM}[1])$
- Rect.hack:  
Draws a rectangle of RAM[0] rows of 16 pixels each.

### ComputerMax.tst

```
load Computer.hdl,
output-file ComputerMax.out,
compare-to ComputerMax.cmp,
output-list time reset ARegister[] DRegister[] PC[]
          RAM16K[0] RAM16K[1] RAM16K[2];

// Loads a Hack program (that executes R2 = max(R0,R1))
ROM32K load Max.hack,

// Test 1: computes max(3,5)
set RAM16K[0] 3,
set RAM16K[1] 5,
output;
repeat 14 {
    tick, tock, output;
}

// Resets the PC
set reset 1,
tick, tock, output;

// Test 2: computes max(23456,12345)
set reset 0,
set RAM16K[0] 23456,
set RAM16K[1] 12345,
output;
repeat 14 {
    tick, tock, output;
}
```

# Testing the computer chip

---

## Testing logic:

- Load `Computer.hdl` into the hardware simulator
- Load a Hack program into the ROM32K chip-part
- Run the clock enough cycles to execute the program

## Test programs


- `Add.hack`:  
 $\text{RAM}[0] \leftarrow 2 + 3$
- `Max.hack`:  
 $\text{RAM}[2] \leftarrow \max(\text{RAM}[0], \text{RAM}[1])$



`Rect.hack`:

Draws a rectangle of  $\text{RAM}[0]$  rows of 16 pixels each.


`Rect.hack` output:

 

## Test script


- `ComputerRect.tst`
- Inspect it, and understand the testing logic.

# What's next?

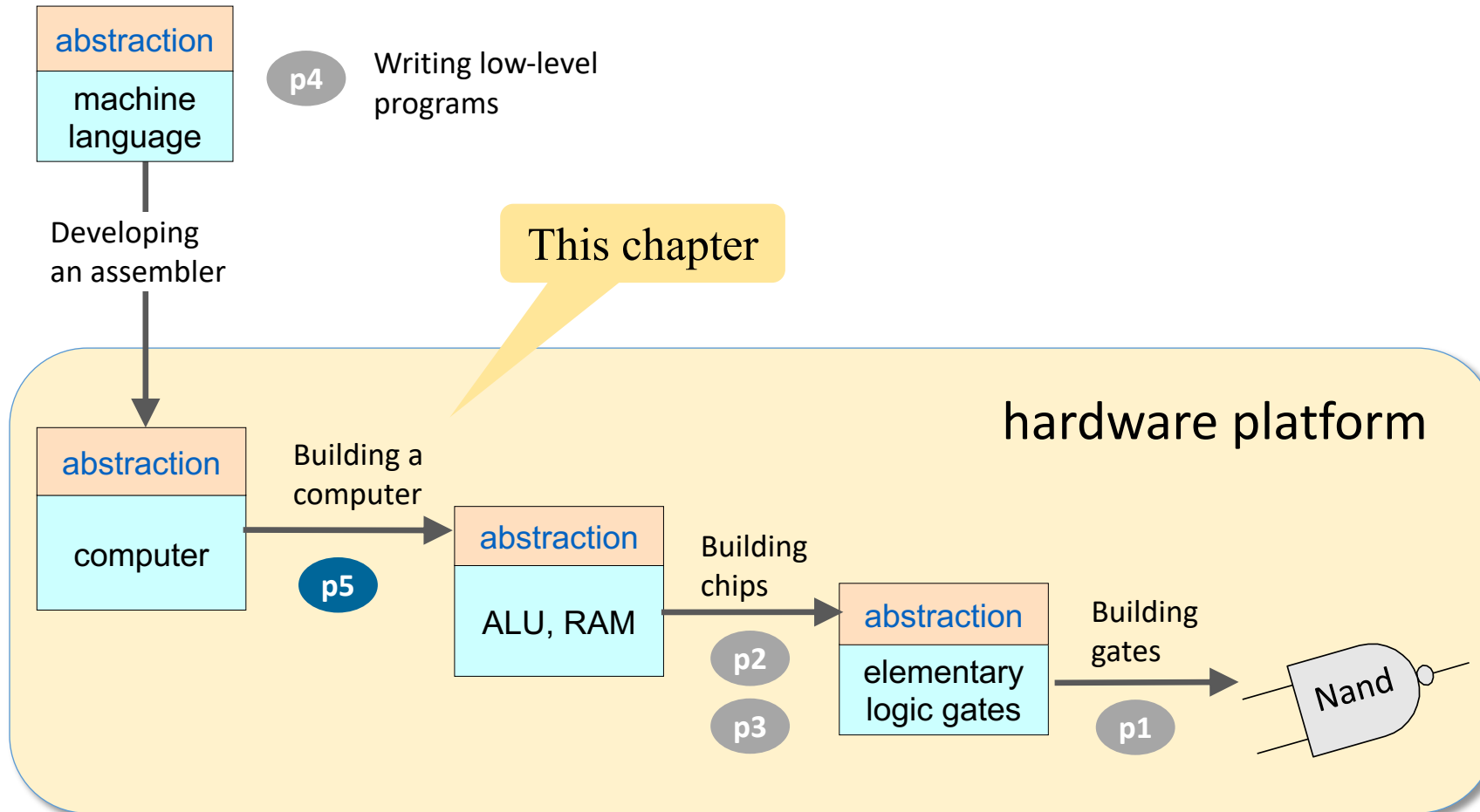




# What's next?

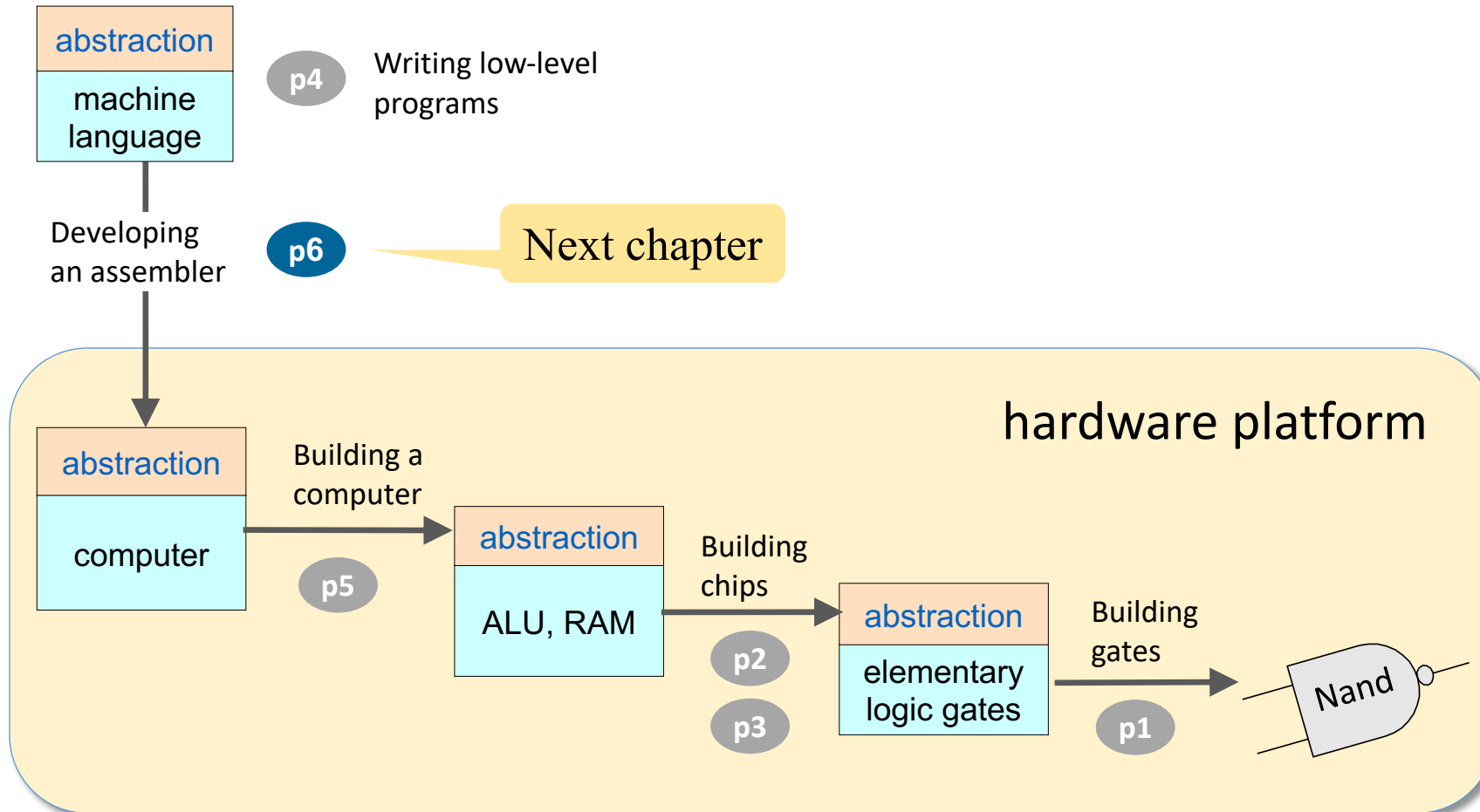

# End note: Memory hierarchy

---

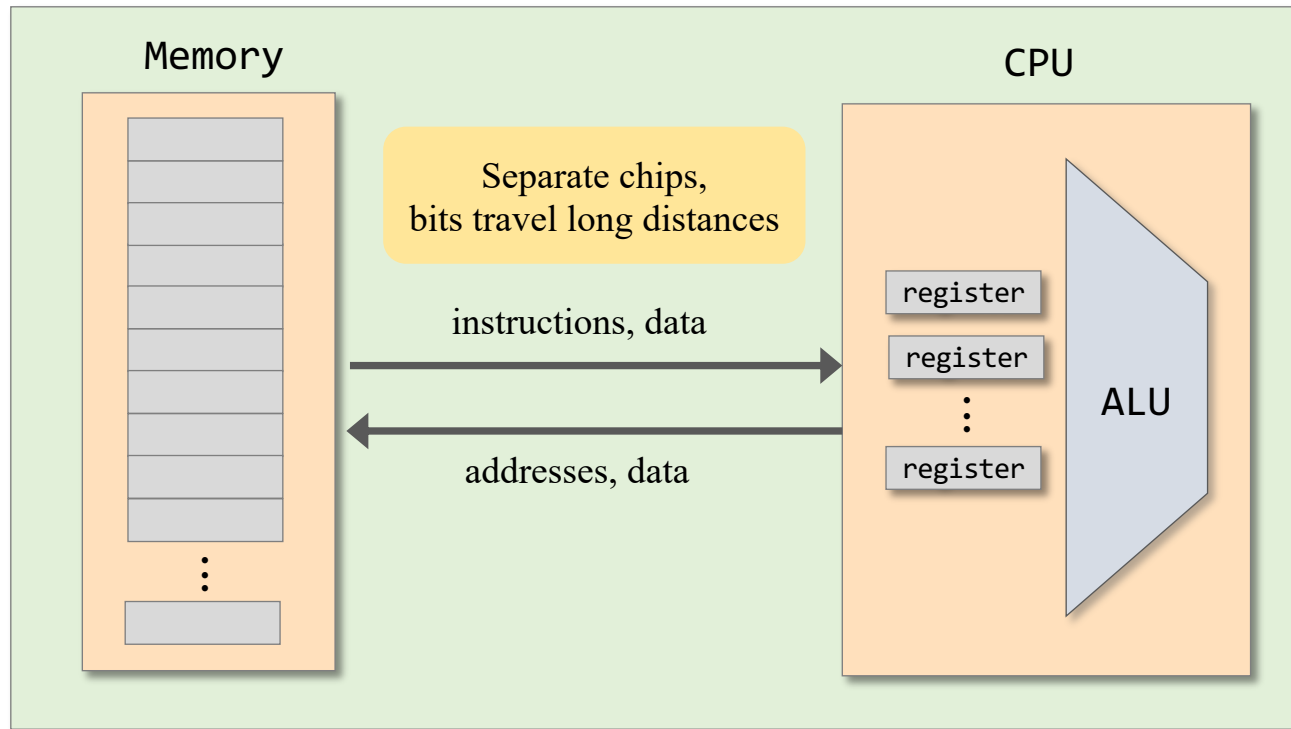


## Challenges

- Slow access time
- Limited memory space

# End note: Memory hierarchy

---

 


## Challenges

- Slow access time
- Limited memory space

## Typical solutions

- Cache memory
- External storage

## End note: Memory hierarchy

 


Memory hierarchy:

← more storage space, slower access time

## End note: Memory hierarchy

---

 

- Mass storage and cache memory are possible *extensions*
- The basic Hack computer is built without them.